

Circuits from the Lab™
Reference Circuits

Circuits from the Lab™ reference circuits are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0272.

Devices Connected/Referenced	
AD8065	High Performance, 145 MHz FASTFET™ Op Amp
AD8475	Precision, Selectable Gain, Fully Differential Funnel Amp
AD9629-20	12-Bit, 20 MSPS, 1.8 V ADC
ADR441	Ultralow Noise, LDO XFET® 2.5 V Voltage Reference with Current Sink and Source

2 MHz Bandwidth PIN Photodiode Preamp with Dark Current Compensation

EVALUATION AND DESIGN SUPPORT

Circuit Evaluation Boards

[CN-0272 Circuit Evaluation Board \(EVAL-CN0272-SDPZ\)](#)
[System Demonstration Platform \(EVAL-SDP-CB1Z\)](#)

Design and Integration Files

[Schematics, Layout Files, Bill of Materials](#)

CIRCUIT FUNCTION AND BENEFITS

The circuit shown in Figure 1 is a high speed photodiode signal conditioning circuit with dark current compensation. The system converts current from a high speed silicon PIN photodiode and drives the inputs of a 20 MSPS analog-to-digital converter (ADC). This combination of parts offers spectral sensitivity from 400 nm to 1050 nm with 49 nA of photocurrent sensitivity, a dynamic range of 91 dB, and a bandwidth of 2 MHz. The signal conditioning circuitry of the system consumes only 40 mA of current from the ± 5 V supplies making this configuration suitable for portable high speed, high resolution light intensity applications, such as pulse oximetry.

Other suitable applications for this circuit are as an analog opto-isolator. It can also be adapted to applications that require larger bandwidth and less resolution such as adaptive speed control systems.

This circuit note discusses the design steps needed to optimize the circuit shown in Figure 1 for a specific bandwidth including stability calculations, noise analysis, and component selection considerations.

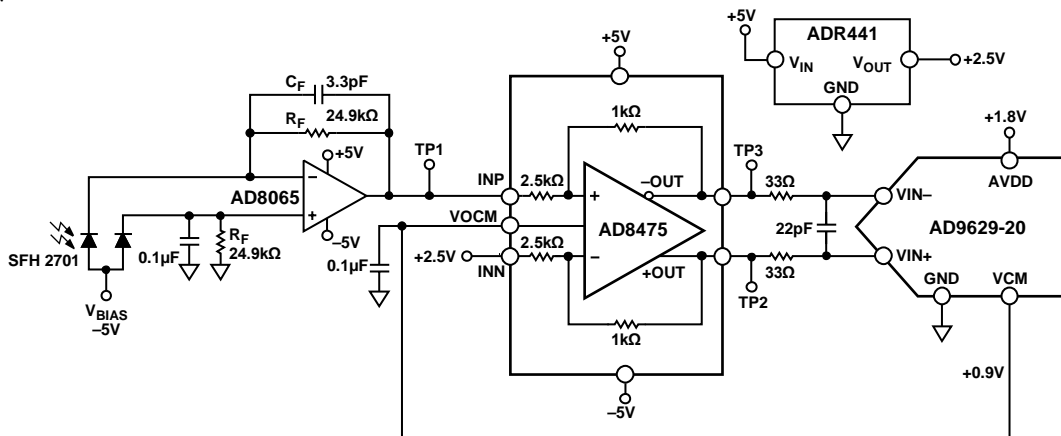


Figure 1. Photodiode Preamp System with Dark Current Compensation (Simplified Schematic: All Connections and Decoupling Not Shown)

Rev. B

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

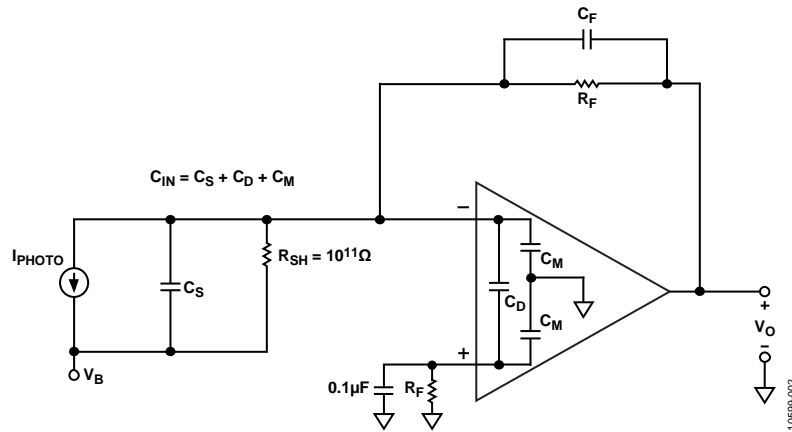


Figure 2. Wideband Photodiode Preamp Equivalent Circuit for AC and Noise Analysis

CIRCUIT DESCRIPTION

Component Selection

Photodiodes are high impedance sensors used to detect the intensity of light. Photodiodes do not have internal gain but can operate at much higher light levels than other light detectors.

Photodiodes operate either with zero bias (photovoltaic mode) or with a reverse bias (photoconductive mode). The most precise linear operation is obtained in the photovoltaic mode, while higher switching speeds are realizable when the diode is operated in the photoconductive mode at the expense of linearity. Under these reverse bias conditions, a small amount of current called dark current flows even when there is no illumination. The dark current error can be cancelled using a second photodiode of the same type in the noninverting input of the op amp as is shown in Figure 1.

Three factors influence the response time of a photodiode

- The charge collection time of the carriers in the depleted region of the photodiode
- The charge collection time of the carriers in the undepleted region of the photodiode
- The RC time constant of the diode circuit combination

Because the junction capacitance is dependent on the diffused area of the photodiode and the applied reverse bias, faster rise times are obtained with smaller diffused area photodiodes and larger applied reverse biases. The junction capacitance for the SFH 2701 PIN photodiode used in the CN-0272 circuit note is 3 pF typical, 5 pF maximum for 0 V bias. The typical capacitance is 2 pF for 1 V reverse bias and 1.7 pF for 5 V reverse bias. Measurements in the circuit were all taken with a reverse bias of 5 V.

Figure 2 shows an I/V converter with an electrical model of a photodiode. The basic transfer function is

$$V_{OUT} = \frac{I_{PHOTO} \times R_F}{1 + sC_F R_F}$$

Where I_{PHOTO} is the output current of the photodiode, and the parallel combination of R_F and C_F sets the signal bandwidth. Ideally, all of the output current from the photodiode passes through R_F , but all op amps have input bias currents that introduce errors on the output. Op amps with picoamps of input bias current and low input offset voltages are preferred to minimize the error. The AD8065 has only 2 pA of input bias current and only 400 μ V of input offset voltage.

The circuit is designed to have a full scale output of 5 V with a maximum photodiode current of 200 μ A. This determines the value of the feedback resistor to be

$$R_F = 5 \text{ V} / 200 \text{ } \mu\text{A} = 24.9 \text{ k}\Omega$$

The stable bandwidth attainable with this preamp is a function of R_F , the gain bandwidth product of the amplifier (65 MHz), and the total capacitance at the amplifier's summing junction, C_{IN} . For this circuit, the SFH 2701 diode (OSRAM Opto Semiconductors GmbH) has a maximum capacitance of $C_D = 5$ pF. The AD8065 common-mode input capacitance is $C_M = 2.1$ pF, and the differential-mode input capacitance is $C_D = 4.5$ pF. Therefore, the total input capacitance is $C_{IN} = 11.6$ pF.

It can be shown that the signal bandwidth resulting in a 45° phase margin, $f_{(45)}$, is defined by

$$f_{(45)} = \sqrt{\frac{f_{CR}}{2\pi \times R_F \times C_{IN}}} = \sqrt{\frac{65 \text{ MHz}}{2\pi \times 24.9 \text{ k}\Omega \times 11.6 \text{ pF}}} \\ = 5.7 \text{ MHz}$$

Because the maximum attainable bandwidth is larger than the intended bandwidth, the AD8065 is a good candidate for the application, which is largely due to its large ratio of f_{CR} to C_{IN} .

R_F and C_{IN} produce a pole in the loop transfer function of the amplifier that can result in peaking and instability (see Figure 3). Adding C_F creates a zero in the loop transfer function that compensates for the effect of the pole and reduces the signal bandwidth.

 


Figure 3. Compensation for Input Capacitance

The value of C_F that produces 2 MHz of bandwidth with the selected value of R_F is

$$C_F = \frac{1}{2\pi R_F f_2} = \frac{1}{2\pi \times 24.9 \text{ k}\Omega \times 2 \text{ MHz}} = 3.3 \text{ pF}$$

To determine if 3.3 pF is enough capacitance to stabilize the system, calculate the amount of capacitance needed to obtain 45° of phase margin. The value of C_F that produces $f_{(45)}$ can be shown as

$$C_F = \sqrt{\frac{C_{IN}}{2\pi \times R_F \times f_{CR}}} = \sqrt{\frac{11.6 \text{ pF}}{2\pi \times 24.9 \text{ k}\Omega \times 65 \text{ MHz}}} = 1.1 \text{ pF}$$

Because the intended value of 3.3 pF is larger than the minimum value of 1.1 pF, the system is stable because increasing the capacitance increases the amount of phase margin.

Noise Analysis

Now that the components are selected, how much resolution is needed to convert the signal must be determined. As in most noise analyses, only the key contributors need to be identified. Noise sources combine in an RSS manner; therefore, any single noise source that is at least three-to-four times larger than any of the others dominates.

In the case of the photodiode preamp, the dominant sources of output noise are the input voltage noise of the op amp and the feedback resistor noise. The input current noise of the FET-input op amp is negligible. The shot noise of the photodiode (caused by reverse bias) is negligible because of the filtering effect of the shunt capacitance.

The resistor noise is calculated using the Johnson noise formula.

$$V_{R_F} RTO = \sqrt{4kTR_F \times 1.57 f_2} = 36 \mu\text{V rms}$$

where:

k is Boltzmann's constant ($1.38 \times 10^{-23} \text{ J/K}$).

T is the absolute temperature in Kelvin.

The factor of 1.57 converts the approximate single-pole bandwidth into the equivalent noise bandwidth.

Note that the 0.1 μF capacitor on the positive input of the preamp eliminates the high frequency noise produced by the second R_F resistor used to cancel the effects of bias current.

The primary source of output noise is due to the input voltage noise and the high frequency noise gain peaking that occurs between f_1 and f_{CR} . If it is assumed that the output noise is constant over the entire range of frequencies and the maximum value for the ac noise gain is used, then

$$V_N RTO = V_N \left(1 + \frac{C_{IN}}{C_F} \right) \sqrt{1.57 f_2} = 56 \mu\text{V rms}$$

where V_N is the input voltage noise of the amplifier (7 nV/ $\sqrt{\text{Hz}}$).

The total rms noise referred to the output is then the RSS value of the two components

$$\text{Total RTO Noise} = \sqrt{(36)^2 + (56)^2} = 67 \mu\text{V rms}$$

The total output dynamic range of the preamp can be calculated by dividing the full scale output signal (5 V) by the total output rms noise (67 $\mu\text{V rms}$) and converting it to decibels, yielding approximately 97 dB.

$$\text{Dynamic Range} = 20 \log(5 \text{ V} / 67 \mu\text{V}) = 97 \text{ dB}$$

ADC Selection

Because the amount of noise output by the amplifier is known the maximum number of bits that can be resolved can now be calculated by dividing the full scale output by the rms noise.

$$\text{Total RMS LSBs} = 5 \text{ V} / 67 \mu\text{V} = 74,627$$

The number of rms LSBs can be converted into effective resolution.

$$\text{Effective Resolution} = \log_2(74,627) = 16.19 \text{ Bits}$$

Noise-free code resolution can be obtained by subtracting 2.7 bits from effective resolution.

$$\begin{aligned} \text{Noise-Free Code Resolution} &= \text{Effective Resolution} - 2.7 \text{ Bits} \\ &= 16.19 \text{ Bits} - 2.7 \text{ Bits} \\ &= 13.49 \text{ Bits} \end{aligned}$$

Depending on the end application, 13 bits may be more resolution than is actually needed. Because the intended application does not require this amount of resolution, it has been confirmed that the system meets the design requirements with 12 bits.

If the LSB size (in current) is smaller than the amount of dark current, as mentioned earlier, the dark current can be canceled using a second photodiode of the same type in the noninverting input of the op amp. For example, if 16 bits of resolution is needed, the amount of photocurrent detected is

$$I_{LSB} = \frac{I_{PHOTO}}{2^N} = \frac{200 \mu\text{A}}{2^{16}} = 3 \text{ nA}$$

Since the maximum amount of dark current that flows in the SFH 2701 is specified at 5 nA, dark current compensation is needed in a 16-bit design.

This application uses a 12-bit ADC; therefore, the LSB size is 49 nA, and it does not require dark current compensation.

If the bandwidth is 2 MHz, a reasonable guideline is to select an ADC with a sampling rate 10 times greater or more. This means the ideal ADC must sample at a rate of 20 MSPS with 12 bits of resolution.

The AD9629-20 is a good candidate because it is a 20 MSPS ADC with 12 bits of resolution. However, it requires differential inputs, and the 5 V p-p single-ended signal must be converted to a 2 V p-p differential signal. This is easily accomplished by using the AD8475 differential funnel amplifier, which simplifies the single-ended-to-differential conversion, and provides common-mode level shifting and precision attenuation.

The AD8475 has only a 500 μV maximum output offset, a 10 nV/ $\sqrt{\text{Hz}}$ differential output noise, and -112 dB total harmonic distortion plus noise (THD + N).

The AD8475 can support a maximum output voltage of 2 V p-p up to 10 MHz, which is well within the design requirement of 2 MHz.

The gain of the AD8475 was determined by the analog input span of the AD9629-20 (2 V p-p) and the full scale output of the AD8065 (5 V p-p).

$$\text{Gain} = 2 \text{ V p-p} / 5 \text{ V p-p} = 0.4$$

An on-chip, common-mode voltage of 0.9 V is included in the AD9629-20 and is available from the VCM pin. This pin drives the VCM pin of the AD8475 with the common-mode voltage of 0.9 V.

It is important to include the noise contribution of the AD8475 in this system. This is calculated by first multiplying the output noise of the AD8065 (67 μV rms) by the gain of the AD8475 to get the contribution due to the AD8065.

$$\begin{aligned} \text{Noise at AD8475 Output due to Noise of AD8065} &= \\ 0.4 \times 67 \mu\text{V rms} &= 27 \mu\text{V rms} \end{aligned}$$

The output noise due to the AD8475 is calculated by multiplying the output noise density (10 nV/ $\sqrt{\text{Hz}}$) by the square root of the bandwidth set by the output filter.

$$\text{Output Filter BW} = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 66 \Omega \times 22 \text{ pF}} = 110 \text{ MHz}$$

Noise at AD8475 Output After Filter =

$$10 \text{ nV}/\sqrt{\text{Hz}} \times \sqrt{(1.57 \times 110 \text{ MHz})} = 131 \mu\text{V rms}$$

The total noise at the output of the AD8475 after the filter is calculated by taking the RSS value of the two components is

$$\text{Total Noise} = \sqrt{(27)^2 + (131)^2} = 134 \mu\text{V rms}$$

With the noise contribution of the AD8475 incorporated into the calculations, the number of bits that can be resolved can be confirmed, and the total dynamic range can be calculated.

$$\text{Total RMS LSBs} = 5 \text{ V} / 134 \mu\text{V} = 37,313$$

$$\text{Effective Resolution} = \log_2(37,313) = 15.19 \text{ Bits}$$

$$\begin{aligned} \text{Noise-Free Code Resolution} &= \text{Effective Resolution} - 2.7 \text{ Bits} \\ &= 15.19 \text{ Bits} - 2.7 \text{ Bits} \\ &= 12.49 \text{ Bits} \end{aligned}$$

$$\text{Dynamic Range} = 20 \log(5 \text{ V} / 134 \mu\text{V}) = 91 \text{ dB}$$

Test Results

A laser diode was used to drive the D1 photodiode and generate a current. Photodiode D2 is used for dark current compensation and is covered with an optically opaque epoxy (EPO-TEK® 320) to prevent output current from D2 when D1 is excited.

By forcing the photodiode to drive a larger than expected current, the approximate maximum rise and fall time of the AD8065 was 72 ns (see Figure 4).

 


Figure 4. Pulse Response by Overdriving the Photodiode

A more realistic rise and fall time of the system can be measured by moving the position of the laser diode so that it does not overdrive the photodiode current beyond 200 μ A. Figure 5 shows the measured rise and fall time of the AD8065 to be 282 ns and 290 ns, respectively. It is important to note that there is no ringing after the laser diode has turned off in both test cases because there is sufficient phase margin.

 


Figure 5. Pulse Response of Laser Diode

Now that the response of the system to a pulse of bright light has been tested, how the system responds to high speed changes in light intensity can be tested. An Agilent 33250A function generator was used to drive a laser diode with a 2 MHz sine wave. Figure 6 shows that the output of the AD8065 was able to successfully detect the small changes in light intensity, and Figure 7 shows a screenshot of the CN0272 Evaluation Software successfully receiving conversion data from the AD9629-20 ADC and plotting the data in a chart.

 


Figure 6. Output of AD8065 Using a Varying Light Source

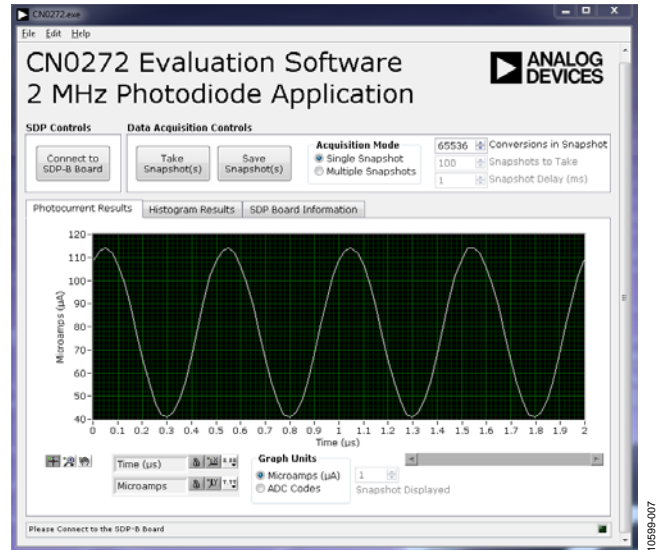


Figure 7. Screenshot of CN0272 Evaluation Software Digitizing a 2 MHz Varying Light Source

A complete design support package for this circuit note can be found at <http://www.analog.com/CN0272-DesignSupport>.

Applications in Pulse Oximetry

A pulse oximeter is a medical device used for continuously measuring the percentage of hemoglobin (Hgb) saturated with oxygen and the pulse rate of a patient. Hemoglobin carrying oxygen (oxyhemoglobin) absorbs light in the infrared region (940 nm) of the spectrum; hemoglobin that is not carrying oxygen (deoxyhemoglobin) absorbs visible red light (650 nm). The percentage of oxygen in the body is determined by calculating the ratio between these two intensities of light.

In a pulse oximeter, two LEDs (one emitting red light and the other emitting infrared light) are rapidly and sequentially excited by two current sources and a photodiode is used to detect the intensity of the light from the LEDs. The circuit shown in Figure 1 can be synchronized with an LED current sink circuit, such as the CN-0125, to capture the light from each LED as it transmits through the tissue

COMMON VARIATIONS

The components selected were optimized for noise and cost; however, other combinations can be substituted.

Other suitable dual supply amplifiers are the [ADA4817-1](#) and [ADA4637-1](#). If single supply operation is required, the [AD8605](#) or the [AD8615](#) are suggested. These amplifiers all have less than 2 pA of input bias current, less than 400 μ V of input offset, and more than 10 MHz of unity-gain bandwidth products.

For applications requiring 100 MHz of bandwidth or greater, such as adaptive speed control, the combination of the [ADA4817-1](#) *FastFET* amplifier, the [ADA4932-1](#) low power differential ADC driver, and the 12-bit, 210 MSPS [AD9634-210](#) ADC are suggested.

The [ADA4817-1](#) has a high gain bandwidth product of 400 MHz and extremely small input capacitance of 1.4 pF. This makes the amplifier ideal for wideband transimpedance applications.

The [ADA4932-1](#) driver can maintain 2 V p-p outputs up to 360 MHz, which is sufficient for the [AD9634-210](#) ADC.

CIRCUIT EVALUATION AND TEST

This circuit uses the [EVAL-CN0272-SDPZ](#) circuit board and the [EVAL-SDP-CB1Z](#) SDP-B System Demonstration Platform controller board. The two boards have 120-pin mating connectors, allowing for the quick setup and evaluation of the performance of the circuit. The [EVAL-CN0272-SDPZ](#) board contains the circuit to be evaluated, as described in this note, and the SDP-B controller board is used with the [CN0272 Evaluation Software](#) to capture the data from the [EVAL-CN0272-SDPZ](#) circuit board.

Equipment Needed

The following equipment is needed:

- A PC with a USB port and Windows® XP (32 bit), Windows Vista®, or Windows® 7
- The [EVAL-CN0272-SDPZ](#) circuit board
- The [EVAL-SDP-CB1Z](#) SDP-B controller board
- The [CN-0272 SDP Evaluation Software](#)
- The [EVAL-CFTL-6V-PWRZ](#) dc power supply or equivalent 6 V/1 A bench supply
- A light source between 400 nm to 1050 nm

Getting Started

Load the evaluation software by placing the CN0272 evaluation software into the CD drive of the PC. Using **My Computer**, locate the drive that contains the evaluation software.

Functional Block Diagram

See Figure 1 for the circuit block diagram and the [EVAL-CN0272-SDPZ-PADSSchematic-RevC.pdf](#) file for the complete circuit schematic. This file is contained in the [CN-0272 Design Support Package](#).

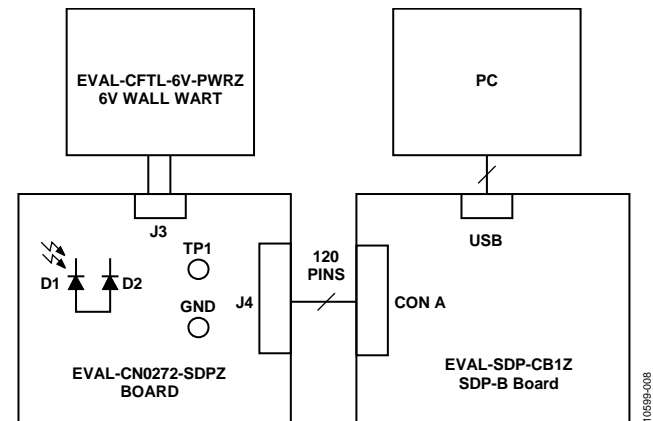


Figure 8. Test Setup Block Diagram

Setup

Connect the 120-pin connector on the [EVAL-CN0272-SDPZ](#) circuit board to the CON A connector on the [EVAL-SDP-CB1Z](#) controller board (SDP-B). Use nylon hardware to firmly secure the two boards, using the holes provided at the ends of the 120-pin connectors. With power to the supply off, connect a 6 V power supply to the +6 V and GND pins on the board. If available, a 6 V wall wart can be connected to the barrel connector on the board and used in place of the 6 V power supply. Connect the USB cable supplied with the SDP-B board to the USB port on the PC. Do not connect the USB cable to the Mini-USB connector on the SDP-B board at this time.

Test

Apply power to the 6 V supply (or wall wart) connected to the [EVAL-CN0272-SDPZ](#) circuit board. Launch the evaluation software and connect the USB cable from the PC to the Mini-USB connector on the SDP-B board.

Once USB communications are established, the SDP-B board can be used to send, receive, and capture parallel data from the [EVAL-CN0272-SDPZ](#) board.

Figure 9 shows a photo of the [EVAL-CN0272-SDPZ](#) evaluation board connected to the SDP board. Information regarding the SDP-B board can be found in the [SDP-B User Guide](#).

Note that photodiode D2 is used for dark current compensation and is covered with an optically opaque epoxy (EPO-TEK 320) to prevent output current from D2 when D1 is excited.

Information and details regarding test setup and calibration, and how to use the evaluation software for data capture can be found in the [CN-0272 Software User Guide](#).

 


Figure 9. EVAL-CN0272-SDPZ Evaluation Board Connected to the EVAL-SDP-CB1Z SDP-B Board

106599-009

Connectivity for Prototype Development

The EVAL-CN0272-SDPZ evaluation board is designed to use the EVAL-SDP-CB1Z SDP-B board; however, any microprocessor can be used to interface to the parallel peripheral interface (PPI) of the AD9629-20. In order for another controller to be used with the EVAL-CN0272-SDPZ evaluation board, software must be developed by a third party.

There are existing interposer boards that can be used to interface to the Altera and Xilinx field programmable gate arrays (FPGAs). The BeMicro SDK board from Altera can be used with the BeMicro SDK/SDP interposer using Nios Drivers. Any Xilinx evaluation board that features the FMC connector can be used with the FMC-SDP Interposer board.

LEARN MORE

CN-0272 Design Support Package:

<http://www.analog.com/CN0272-DesignSupport>

SDP-B User Guide

Ardizzoni, John. *A Practical Guide to High-Speed Printed-Circuit-Board Layout*, Analog Dialogue 39-09, September 2005.

Kester, Walt, Wurcer, Scott, Kitchin, Chuck. *High Impedance Sensors*, Practical Design Techniques for Sensor Signal Conditioning, Section 5, 1999.

MT-004 Tutorial, *The Good, the Bad, and the Ugly Aspects of ADC Input Noise—Is No Noise Good Noise?* Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of “AGND” and “DGND”*, Analog Devices.

MT-035, *Op Amp Inputs, Outputs, Single-Supply, and Rail-to-Rail Issues*, Analog Devices.

MT-036 Tutorial, *Op Amp Output Phase-Reversal and Input Over-Voltage Protection*, Analog Devices.

MT-068 Tutorial, *Difference and Current Sense Amplifiers*, Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.

CN-0125, *High Precision, Low Power, Low Cost Pulse Oximeter Infrared and Red Current Sinks Using the ADA4505-2 10 μ A Zero Input Crossover Distortion Op Amp, ADR1581 Precision Shunt Voltage Reference, and ADG1636 Dual SPDT Switches*, Analog Devices.

DiffAmpCalc™: Differential Amplifier Calculator

Analog Photodiode Wizard

Analog Devices Pulse Oximetry Products

SFH-2701 PIN Photodiode, OSRAM Opto Semiconductors GmbH

Photodiode Characteristics and Applications, Application Note, OSI Optoelectronics, 12525 Chadron Ave, Hawthorne, CA 90250

Data Sheets and Evaluation Boards

CN-0272 Circuit Evaluation Board (EVAL-CN0272-SDPZ)

System Demonstration Platform (EVAL-SDP-CB1Z)

AD8065 Datasheet

AD8475 Datasheet

ADR441 Datasheet

AD9629-20 Datasheet

REVISION HISTORY**11/13—Rev. A to Rev. B**

Changes to Figure 3.....3

Changes to Figure 7.....5

12/12—Rev. 0 to Rev. A

Changes to Test Section.....6

11/12—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

X-ON Electronics

Largest Supplier of Electrical and Electronic Components

Click to view similar products for [Other Development Tools](#) category:

Click to view products by [Analog Devices](#) manufacturer:

Other Similar products are found below :

[DS100BR410EVK-4/NOPB](#) [BK0004](#) [BK0012](#) [SN65MLVD2-3EVM](#) [DS80EP100-EVK](#) [MAX9684EVKIT#](#) [MAX4952AEVKIT+](#) [ESD-EVM-001](#) [MAX14842EVKIT+](#) [EVAL01-HMC749LC3C](#) [410-320](#) [TPD6F002-Q1EVM](#) [TS9002DB](#) [DS80PCI800EVK/NOPB](#) [118777-HMC722LC3C](#) [118777-HMC723LC3C](#) [118777-HMC678LC3C](#) [DC1765A-A](#) [125614-HMC851LC3C](#) [TPD1E05U06DPYEVM](#) [SN65LVDM31-32BEVM](#) [DC2062A-A](#) [NB4N855SMEVB](#) [LMH6321MR-EVAL/NOPB](#) [EVAL01-HMC747LC3C](#) [4537](#) [DK-M3F-1.8-TRK-1.5-S](#) [DK-M3-FS-1.8-1.5-M12/16](#) [DK-M3L-1.8-TRK-6.0-S](#) [DK-M3-LS-1.8-6](#) [ADALM1000](#) [ADALP2000](#) [EVAL-CN0202-SDPZ](#) [EVAL-CN0203-SDPZ](#) [EVAL-CN0204-SDPZ](#) [EVAL-CN0209-SDPZ](#) [EVAL-CN0225-SDPZ](#) [EVAL-CN0229-SDPZ](#) [EVAL-CN0251-SDPZ](#) [EVAL-CN0272-SDPZ](#) [EVAL-CN0301-SDPZ](#) [EVAL-CN0325-SDPZ](#) [EVAL-CN0355-PMDZ](#) [EVAL-CN0364-SDPZ](#) [EVAL-SDP-CB1Z](#) [EVAL-SDP-CS1Z](#) [DS1964SEVKIT#](#) [MAX14611EVKIT#](#) [MAX22088EVKIT#](#) [MAX4951AEEVKIT+](#)