
# **RS-485 Port Protection Evaluation Board 4**
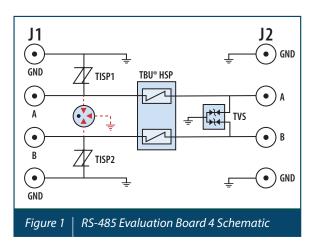
### **INTRODUCTION**

This evaluation board serves as an aid in evaluating circuit protection solutions for RS-485 serial ports. It uses a Bourns® TBU® High-Speed Protector (HSP), a Gas Discharge Tube (GDT) Surge Arrestor and a Transient Voltage Suppressor (TVS) that are designed to meet the required industry standards on RS-485 port interfaces. The recommended Bourns® TBU® HSP solution offers enhanced performance features over competing technologies. These performance features can help engineers improve the surge and transient protection level on RS-485 ports, while allowing them to place the entire circuit protection solution into a smaller PCB area as compared to alternative solutions. The Bourns® RS-485 Evaluation Board 4 measures 35 mm x 25 mm x 0.85 mm, and is manufactured using an FR-4 PCB with nickel-gold pad plating on the top and bottom sides.



Bourns' three previous versions of the RS-485 Evaluation Boards (EVB1, 2 and 3) used the Bourns® Model TBU-CA, which is a single-channel device. Because the RS-485 interface has two lines, this new evaluation board provides further PCB area reduction by utilizing the new Bourns® Model TBU-DF HSP, which is a dual-channel device. This latest evaluation board is the smallest RS-485 evaluation board offering a more compact solution helping designers save valuable PCB real estate.

## HOW TO CONNECT THE EVALUATION BOARD FOR TEST SET-UP

- Connect J1A and J1B to the exposed lines.
- Connect J2A and J2B to the RS-485 IC device.

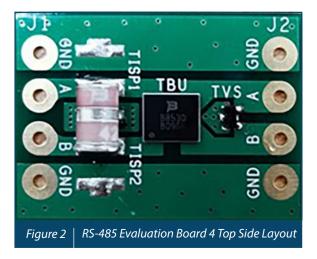


Table 1	RS-485 Evaluation Board 4 Bill of Materials				
No.	Part Number	Qty.	Description	Product	
1	TBU-DF085-300-WH	1	850 V 300 mA Dual Channel Bidirectional TBU® HSP	TBU <sup>®</sup> HSP	
2	2030-42T-SM-RPLF	1	Fast Acting, 3-Electrode 420 V Gas Discharge Tube	GDT	
3	CDS0T23-SM712	1	SOT23 12 V Dual Bidirectional TVS Diode	TVS Diode	

The default configuration of this board uses a TBU<sup>®</sup> HSP, a GDT and a TVS diode. The board allows different configurations:

- One Model 2030-42T-SM-RPLF could be replaced by two Model TISP4350J3BJR-S
- One Model 2030-42T-SM-RPLF could be replaced by two Model TISP4500H3BJR-S
- One Model 2030-42T-SM-RPLF could be replaced by one Model 2036-07-SM-RPLF

### **RS-485 Port Protection Evaluation Board 4**

### **RS-485 EVALBOARD 4 CONFIGURATION**

Protection of RS-485 ports are typically required in three scenarios. The first scenario is for exposed and harsh environments, such as outdoor installations where induced lightning surges are a threat. Customers for these types of applications are familiar with the ITU-T K.20/21/44 recommendations (specifying the 10/700 µs voltage, surge) or with the Telcordia GR-1089-CORE or IEC 61000-4-5 standard (specifying the CWG 8/20 µs current, 1.2/50 µs voltage surges).

The second scenario accommodates long cable runs where multiple lines (data and AC power) are used in the same trucking or cabling. During a fault incidence, the AC power lines may come in contact with the signal lines. These applications require 230 V<sub>AC</sub> tests specified in ITU-T K.20/21/44, or 120 V<sub>AC</sub> tests specified in Telcordia GR-1089-CORE. There are applications with lower voltage application/installation threats, but where the standardized 120 V<sub>AC</sub> or 230 V<sub>AC</sub> tests are still used to test the robustness of the protection solution. The third scenario protects against installation errors and faults. For example,  $12 V_{DC}$  or  $24 V_{DC}$  lines are frequently run together with the signal lines. The cable runs may include other exposed lines that can induce lightning surges onto RS-485 ports. In addition, there is the risk of deliberate and malicious attacks on RS-485 ports by unauthorized users. All of these can typically be taken care of with a protection solution that meets the higher protection levels offered in scenarios one and two.

This evaluation board brief will highlight options for two levels of lightning surges that use a TISP<sup>®</sup> Thyristor Surge Protector for the lower surge level and a GDT for the higher surge level. By varying the chosen voltage, this brief will also demonstrate that AC power cross up to 120 V<sub>AC</sub> or 230 V<sub>AC</sub> can be accommodated by a Bourns<sup>®</sup> Model TBU-DF based RS-485 protection solution.


Table 2       Bourns® TBU® High-Speed Protector (HSP) and Overvoltage Protector (OVP) Combination						
OVP Part Number	OVP Surge Rating	V <sub>DRM</sub> (V)	V <sub>BO</sub> (V) (1000 V/μs)	TBU® HSP Part Number	Surge Capability	AC Power Cross Capability
TISP4350J3BJR-S	800 A, 8/20 μs 350 A, 5/310 μs	275	350	TBU-DF055-300-WH	IEC61000-4-5, Level 4,	120 V <sub>AC</sub>
2030-42T-SM	500 Α, 8/20 μs 150 Α, 5/310 μs	360	850	TBU-DF085-300-WH	4 kV 1.2/50 μs, 42 0hm	230 V <sub>AC</sub>
TISP4500H3BJR-S	200 A, 5/310 μs	350	500	TBU-DF055-300-WH	ITU K.20/21/45 Enhanced Lighting,	230 V <sub>AC</sub>
2036-07-SM	10,000 Α, 8/20 μs 2,000 Α, 5/310 μs	75	750	TBU-DF085-300-WH	6 kV 10/700 μs, 40 0hm	-

Overvoltage Protector (OVP) Selection:

Breakover voltage (V<sub>BO</sub>) or impulse breakdown voltage (V<sub>imp</sub>) of the overvoltage protector (OVP) should be below the maximum Peak Impulse Voltage (V<sub>imp</sub>) of the TBU<sup>®</sup> HSP.

• V<sub>BO</sub> or V<sub>imp</sub> of the OVP should be above the maximum voltage of AC power cross (peak of V<sub>AC</sub>).

### **SURGE CAPABILITY**

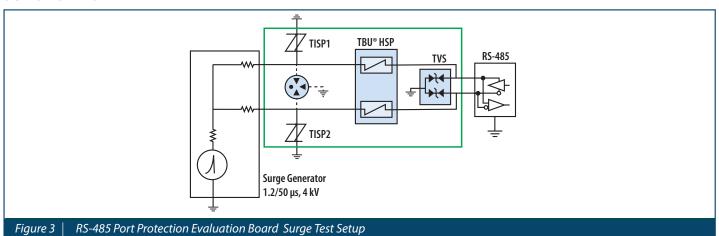

## **RS-485 Port Protection Evaluation Board 4**

Below are graphs of different surge tests performed on Bourns' RS-485 Evaluation Board 4 based on the various standards requirements.

Table 3     Test Results for Bourns	TBU® High-Speed Protector (HSP) and Overvoltage Protector (OVP) Combination			
	TBU <sup>®</sup> HSP & OVP Combination Products			
1 Bourns <sup>®</sup> Model TBU-DF055-300-WH	2 Bourns® Model TISP4350J3BJR-S 1 Bourns® Model CDS0T23-SM712			
Test Results	Surge Capability: IEC61000-4-5 Level 4, 4 kV 1.2/50 μs			
Instance         ∨++         48.88µs         Trig?O         Measure         Vpp         Vpp         Vpp         1:5600         Vpp         1:5600         Vpp         1:5600         Vpp         1:5600         Vpp         1:5600         Vpp         1:5600         2:55.77         Frequencies         2:5.77         Pise Tim         1:52.577         2:3330         Pise Tim         1:52.577         2:3330         Pise Tim         1:52.577         2:3330         2:3330         2:3330         2:3330         2:3330         2:3330         2:3330         2:3330         2:3330         2:3330         2:3330         2:3330         2:3330         3:330<	<ul> <li>current flow into the protected interface.</li> <li>When the line voltage increases to the V<sub>BO</sub> of TISP4350J3BJR-S (350V), TISP4350J3BJR-S will trigger shunt the line to GN</li> <li>Hence, the protected interface is only subject to a very low (300 mA) transient current &lt;1 μs and the interface exposed to low line voltage of 360 V momentarily.</li> </ul>			
H1: TISP4350J3BJR-S Voltage CH2: Surge G Test Results	enerator Output Current Surge Capability: IEC61000-4-5 Level 4, 6 kV 10/700 μs			
Ematatick ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓	<ul> <li>current flow into the protected interface.</li> <li>When the line voltage increases to the V<sub>BO</sub> of TISP4350J3BJR-S (350 V), TISP4350J3BJR-S will trigger shunt the line to GN</li> <li>Hence, the protected interface is only subject to a very low (300 mA) transient current &lt;1 us and the interface exposed to</li> </ul>			

low line voltage of 352 V momentarily.

#### CH1: TISP4350J3BJR-S Voltage CH2: Surge Generator Output Current

CH2 EDGE

@ 100us

1: 312.7ns 2: 3.799us 5DC

Table 4       Test Results for Bourns® TBU® High-Speed Protector (HSP) and Overvoltage Protector (OVP) Combination				
TBU® HSP & OVP Combination Products				
1 Bourns® Model TBU-DF085-300-WH	1 Bourns <sup>®</sup> Model 2030-42T-SM-RPLF	1 Bourns <sup>®</sup> Model CDS0T23-SM712		
Test Results	Surge Capability: IEC61000-4-5 Level 4, 4 kV 1.2/50 μs			
<ul> <li>When the IBU-DF085-300-WH is in the blocking state, the line voltage (Channel 1) increases with the surge, as there is no current flow into the protected interface.</li> <li>When the IBU-DF085-300-WH is in the blocking state, the line voltage (Channel 1) increases with the surge, as there is no current flow into the protected interface.</li> <li>When the line voltage increases to the V<sub>BO</sub> of 2030-42T-SM (850 V), 2030-42T-SM will trigger shunt the line to GND.</li> <li>Hence, the protected interface is only subject to a very low (300 mA) transient current &lt;1 μs and the interface exposed to a low line voltage of 820 V momentarily.</li> </ul>				

#### CH1: 2030-42T-SM-RPLF Voltage CH2: Surge Generator Output Current

Test Results	Surge Capability: IEC61000-4-5 Level 4, 6 kV 10/700 µs
exmans v++ 404.8us Trip? ↑ Messure Vpp 1:5600 2:1598 Vavg 1:-39.40 2:57.7A Frequency 1:-39.40 2:57.7A Frequency 1:-39.40 2:57.7A Rise Time 1:-319.94k 1:-27. 2:0,054k 2:0,055	<ul> <li>current flow into the protected interface.</li> <li>When the line voltage increases to the V<sub>BO</sub> of 2030-42T-SM (850 V), 2030-42T-SM will trigger shunt the line to GND.</li> <li>Hence, the protected interface is only subject to a very low (300 mA) transient current &lt;1 µs and the interface exposed to a low line voltage of 560 V momentarily.</li> </ul>

CH1: 2030-42T-SM-RPLF Voltage CH2: Surge Generator Output Current

## **RS-485 Port Protection Evaluation Board 4**

Table 5       Test Results for Bourns® TBU® High-Speed Protector (HSP) and Overvoltage Protector (OVP) Combination         TBU® HSP & OVP Combination Products				
1 Bourns <sup>®</sup> Model TBU-DF055-300-WH	2 Bourns® Model TISP4500H3BJR-S	1 Bourns® Model CDS0T23-SM712		
Test Results	Surge Capability: IEC61000-4-5 Level 4, 4 kV 1.2/50 µs			
Ministrik         V++ 39,60us         Trig?         Measure           Vpp         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.4960         2.96.06         1.4960           2.96.06         1.192         2.96.06         1.192           2.92         1.192         1.192         2.42800           2.92         1.900         1.900         1.192         1.24200           2.92         1.900         1.900         1.192         1.24200           2.92         1.900         1.900         1.900         1.900           3.990         1.900         1.900         1.900         1.900	<ul> <li>Upon application of the 4 kV (95.2 A) surge (Channel 2), the transient current flowing through TBU-DF055-300-WH increases to trigger TBU-DF055-300-WH quickly (&lt;1 µs).</li> <li>When the TBU-DF055-300-WH is in the blocking state, the line voltage (Channel 1) increases with the surge, as there is no current flow into the protected interface.</li> <li>When the line voltage increases to the V<sub>BO</sub> of TISP4500H3BJR-S (500 V), TISP4500H3BJR-S will trigger shunt the line to GND.</li> <li>Hence, the protected interface is only subject to a very low (300 mA) transient current &lt;1 µs and the interface exposed to a low line voltage of 496 V momentarily.</li> </ul>			
Test Results	Surge Capability: IEC61000	-4-5 Level 4, 6 kV 10/700 μs		
Ministrix         V++         400,0us         Trig?●         Measure           Vpp         1         14640         2         1548           Varg         1         -7.590         2         57.661           Frequenci         1         ?         2         ?           Duty Cycl         1         ?         ?         ?           Rise Time         1         ?         ?         Rise Time           1: 320.0m         2         3.6690         ?         ?         ?           0         1980x         0         CH2         EDE         FOC	<ul> <li>current flow into the protected interface.</li> <li>When the line voltage increases to the V<sub>B0</sub> of TISP4500H3BJR-S (</li> <li>Hence, the protected interface is only subject to a very low (3 low line voltage of 464 V momentarily)</li> </ul>	ne voltage (Channel 1) increases with the surge, as there is no 500 V), TISP4500H3BJR-S will trigger shunt the line to GND.		

CH1: TISP4500H3BJR-S Voltage CH2: Surge Generator Output Current

TBU® HSP & OVP Combination Products				
1 Bourns® Model TBU-DF085-300-WH	1 Bourns <sup>®</sup> Model 2036-07-SM-RPLF	1 Bourns <sup>®</sup> Model CDSOT23-SM712		
Test Results	Surge Capability: IEC61000-4-5 Level 4, 4 kV 1.2/50 μs			
exingrex →++ 48.08us Frig?O , Measure Vpp 1 6480 2 96.08 1 3.330 2 45.18 Duty Cycle 1 ? 2 ? Duty Cycle 1 ? 2 ? Duty Cycle 2 ? Duty Cycle 1 ? 2 ? Rise Time 1 ? 2 ?.169us 0 CH2 EDCE ∫DC 0 2090 0 10us 0 CH2 EDCE ∫DC (30)	current flow into the protected interface. • When the line voltage increases to the V <sub>BO</sub> of 2036-07-SM (7	ne voltage (Channel 1) increases with the surge, as there is no		

#### Surge Capability: IEC61000-4-5 Level 4, 6 kV 10/700 µs **Test Results** Measure Vpp • Upon application of the 6 kV (150 A) surge (Channel 2), the transient current flowing through TBU-DF085-300-WH 5920 150A Vavg increases to trigger TBU-DF085-300-WH quickly (<1 µs). -219mU 57.5A When the TBU-DF085-300-WH is in the blocking state, the line voltage (Channel 1) increases with the surge, as there is no Frequency current flow into the protected interface. ? Duty Cycle 1: ? 2: ? When the line voltage increases to the V<sub>BO</sub> of 2036-07-SM (750 V), 2036-07-SM will trigger shunt the line to GND. Hence, the protected interface is only subject to a very low (300 mA) transient current <1 µs and the interface exposed to a Rise Time 1: ? 2: 4.452us FDC low line voltage of 592 V momentarily. @ 100us O CH2 EDGE

CH1: 2036-07-SM-RPLF Voltage CH2: Surge Generator Output Current

## **RS-485 Port Protection Evaluation Board 4**

### **AC POWER CROSS CAPABILITY**

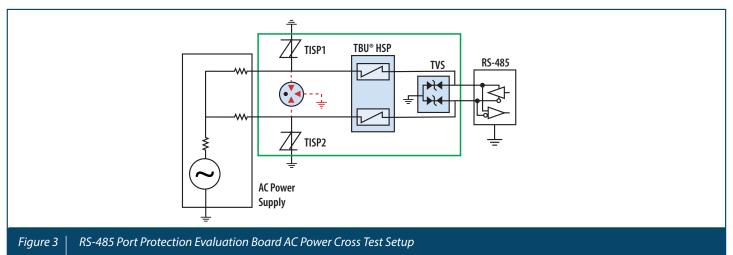


Table 7       Test Results for Bourns® TBU® High-Speed Protector (HSP) and Overvoltage Protector (OVP) Combination				
TBU <sup>®</sup> HSP & OVP Combination Products				
1 Bourns <sup>®</sup> Model TBU-DF055-300-WH	2 Bourns <sup>®</sup> Model TISP4350J3BJR-S	1 Bourns <sup>®</sup> Model CDS0T23-SM712		
Test Results	Surge Capability: AC Power Cross 120 V <sub>AC</sub>			
Ch1 Max Ch2 Max Ch1 192 V M2 200mA M2 00mS A Ch1 55.0 V 0 Nov 2017		JJ3BJR-S (350 V) will maintain high impedance. 1) and line current (Channel 2) increases, Bourns® Model when the line current reaches its I <sub>TRIGGER</sub> (300 mA), preventing ne current (Channel 2) drops to 0 mA after the Bourns® Model		

CH1: A TBU Voltage CH2: CH2: Line A TBU Current

www.bourns.com

### BOURNS

#### EMEA: Tel +36 88 520 390

Email eurocus@bourns.com

Asia-Pacific: Tel +886-2 256 241 17 Email asiacus@bourns.com

Americas: Tel +1-951 781-5500 Email americus@bourns.com

> COPYRIGHT© 2018 • BOURNS, INC. • 8/28 • e/K1901A "TBU" is a registered trademark of Bourns, Inc. in the U.S. and other countries, except Japan. All references to TBU® in this document for use in Japan shall be deemed to be replaced with Bourns® TBU™. "Bourns" and "TISP" are registered trademarks of Bourns, Inc. in the U.S. and other countries.

### **X-ON Electronics**

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Other Development Tools category:

Click to view products by Bourns manufacturer:

Other Similar products are found below :

DS100BR410EVK-4/NOPB BK0004 BK0012 SN65MLVD2-3EVM DS80EP100-EVK MAX9684EVKIT# MAX4952AEVKIT+ ESD-EVM-001 MAX14842EVKIT+ EVAL01-HMC749LC3C 410-320 TPD6F002-Q1EVM TS9002DB DS80PCI800EVK/NOPB 118777-HMC722LC3C 118777-HMC723LC3C 118777-HMC678LC3C DC1765A-A 125614-HMC851LC3C TPD1E05U06DPYEVM SN65LVDM31-32BEVM DC2062A-A NB4N855SMEVB LMH6321MR-EVAL/NOPB EVAL01-HMC747LC3C 4537 DK-M3F-1.8-TRK-1.5-S DK-M3-FS-1.8-1.5-M12/16 DK-M3L-1.8-TRK-6.0-S DK-M3-LS-1.8-6 ADALM1000 ADALP2000 EVAL-CN0202-SDPZ EVAL-CN0203-SDPZ EVAL-CN0204-SDPZ EVAL-CN0209-SDPZ EVAL-CN0225-SDPZ EVAL-CN0229-SDPZ EVAL-CN0251-SDPZ EVAL-CN0272-SDPZ EVAL-CN0301-SDPZ EVAL-CN0325-SDPZ EVAL-CN0355-PMDZ EVAL-CN0364-SDPZ EVAL-SDP-CB1Z EVAL-SDP-CS1Z DS1964SEVKIT# MAX14611EVKIT# MAX22088EVKIT# MAX4951AEEVKIT+