# AN2007-05

## 2ED300E17-SFO

Evaluation Board for 2ED300C17-S/-ST IGBT driver

IFAG AIM PMD ID AE



Never stop thinking

Edition 2008-02-05 Published by Infineon Technologies AG 59568 Warstein, Germany © Infineon Technologies AG 2008. All Rights Reserved.

#### LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

#### Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office (www.infineon.com).

#### Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.



AN2007-01		
<b>Revision History:</b>	2008-02	V1.1
Previous Version:	1.0	
Page	Subjects (major changes since last revision)	
11	Update Table 9	
17	Update IFX order numbers	

Author: Piotr Luniewski IFAG AIM PMD ID AE

## We Listen to Your Comments


Any information within this document that you feel is wrong, unclear or missing at all? Your feedback will help us to continuously improve the quality of this document. Please send your proposal (including a reference to this document) to:

info.power@infineon.com



Table	of Contents	Page
1 1	NTRODUCTION	5
2 [	DESIGN FEATURES	6
2.1 2.2 2.3 2.4	MAIN FEATURES KEY DATA PIN ASSIGNMENT MECHANICAL DIMENSIONS OF THE 2ED300E17-SFO EVALUATION BOARD	6 7
3 A	APPLICATION NOTE	10
3.1 3.2 3.3 3.4 3.5 3.6 3.7 3.8	POWER SUPPLY INPUT LOGIC – PWM SIGNALS FAULT OUTPUT AND RESET DIRECT OR HALF-BRIDGE MODE SELECTION SSD – 'SOFT SHUT DOWN' REFERENCE CURVE AND AND TRIGGER SUPPRESSION THE MINIMUM CIRCUIT FOR PROPER X2 UTILISATION OPERATION WITH MA300E12 OR MA300E17	
4 S	SCHEMATIC, LAYOUT AND BILL OF MATERIAL	14
4.1 4.2 4.3 4.4	SCHEMATIC Assembly drawing Layout Bill of Material	
5 H	HOW TO ORDER EVALUATION DRIVER BOARDS	17

## Part number explanation:

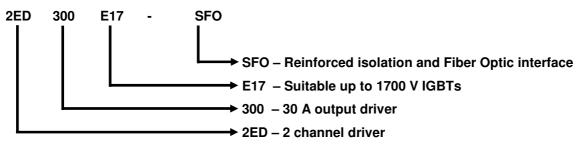



**Page Introduction** 

## 1 Introduction

The 2ED300E17-SFO evaluation board shown in Figure 1 offers basic support for the EiceDRIVER<sup>™</sup> 2ED300C17-S and 2ED300C17-ST IGBT drivers. Enabling embedded driver's functions the evaluation board can be used as platform when power electronic system employing Infineon IGBT modules in 600V, 1200V and 1700V class is being designed. This evaluation board is especially useful together with MA300E12 or MA300E17 as another evaluation boards dedicated to PrimePACK<sup>™</sup> modules in 1200 V and 1700 V voltage class. Exhaustive information about the universal driver set dedicated for PrimePACK<sup>™</sup> modules is available in AN2007-06.

The 2ED300E17-SFO evaluation board is available from Infineon in small quantities. Functions and properties of these parts are described in the datasheet chapter of this document whereas the remaining paragraphs provide information intended to enable the customer to copy, modify and qualify the design for production according to his specific requirements.

The design of the 2ED300E17-SFO was performed with respect to the environmental conditions described in 2ED300C17-S /-ST EiceDRIVER<sup>™</sup> datasheet. The requirements for leadfree reflow soldering have been considered when components were selected. The design was tested as described in this documentation but not qualified regarding manufacturing and operation in the whole operating ambient temperature range or lifetime.

The boards provided by Infineon are subjected to functional testing only.

Due to their purpose evaluation boards are not subjected to the same procedures regarding Returned Material Analysis (RMA), Process Change Notification (PCN) and Product Withdraw (PWD) as regular products.

See Legal Disclaimer and Warnings for further restrictions on Infineon warranty and liability.

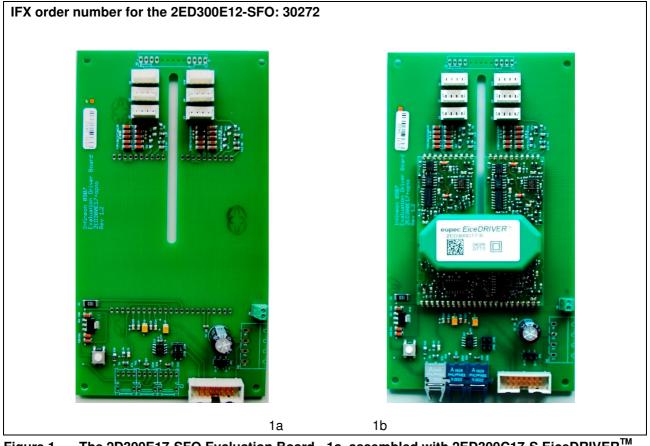


Figure 1 The 2D300E17-SFO Evaluation Board - 1a, assembled with 2ED300C17-S EiceDRIVER<sup>™</sup> and Fiber Optic devices – 1b



## Page Design features

## 2 Design features

Electric features of the evaluation board and mechanic dimensions including necessary interface connections are presented in following sections.

## 2.1 Main features

The 2ED300E17-SFO evaluation board offers the following features:

- Dual channel IGBT driver together with 2ED300C17-S /-ST EiceDRIVER™
- Electrically suitable for 600 V, 1200 V and 1700 V IGBT modules like: IHM, 62mm, EconoDUAL<sup>™</sup>, EconoPACK+<sup>™</sup>
- Electrically and mechanically suitable for PrimePACK<sup>™</sup> modules family when used with MA300E12 or MA300E17
- Electrical and optical interface
- Under Voltage Lockout
- Short circuit protection
- PCB is designed to fulfil the requirements of IEC61800-5-1, pollution degree 2, overvoltage category III

## 2.2 Key data

All values given in the table bellow are typical values, measured at  $T_A = 25$  °C

#### Table 1 General key data and characteristic values

Parameter	Value	Unit
V <sub>DC</sub> – primary DC voltage supply	+15 (±1)	V
I <sub>DC</sub> – primary DC current drawn (idle mode)	100	mA
<b>f</b> <sub>s</sub> – max. PWM signal frequency for A and B channel <sup>1</sup>	60	kHz
<b>T</b> <sub>op</sub> – operating temperature (design target)	-40+85	°C
T <sub>sto</sub> – storage temperature (design target)	-40+85	S

#### Table 2 Key data and characteristic values for electrical interface

Parameter	Value	Unit
$V_{IN A} / V_{IN B} - PWM$ signals for A and B driver channel (active high)	0 / +V <sub>DC</sub>	V
V <sub>FAULT</sub> – FAULT detection output (active high)	0 / + V <sub>DC</sub>	V
IFAULT – max. FAULT detection output load current (open collector output)	20	mA
V <sub>RST</sub> – reset input (active high)	0 / + V <sub>DC</sub>	V

#### Table 3 Key data and characteristic values for optical interface

Parameter	Value	Unit
PWM signals for A and B driver channel (IGBT ON command)	Light ON	
FAULT detection output (fault report)	Light ON	

<sup>&</sup>lt;sup>1</sup> Given switching frequency is limited by driver capabilities. The maximum switching frequency for every IGBT module type should be calculated separately. Limitation factors are: max. DC/DC output power of 4 W per channel and max. PCB board temperature measured around gate resistors placed on separated board close to IGBT module.



#### Page Design features

## 2.3 Pin assignment

All external driver electrical control signals should be applied to connector X1 as shown on Fig. 2 and listed in Table 4. Needed voltage power supply for a driver can be connected to X1 but also to X6 or X5 when convenient (Table 5).

Connector X2 offers 2ED300C17-S /-ST EiceDRIVER<sup>TM</sup> necessary signals to drive an IGBT module with minimum number of required external components. The necessary circuit and functionality describes chapter 3.5 and control signals are listed in Table 6. This basic circuit is universal and together with 2ED300C17-S EiceDRIVER<sup>TM</sup> can be used for medium and high power modules when V<sub>CES</sub> module voltage is lower than 1700V.

Connectors: X3, X7, X9 and respectively X4, X8, X10 are in parallel. In practice an additional circuit containing at least amplifier for an IGBT gate signal must be used. This function and additional like: Active Clamping which keeps temporary  $V_{CE}$  overvoltages bellow  $V_{CES}$ ,  $V_{CE}$  desaturation diodes as part of short circuit protection schema, gate resistors and others are successfully implemented into MA300E12 and MA300E17 evaluation boards. As can be simply concluded the MA300EXX boards are electrically fitting to signals described in Table 7 and give working platform when PrimePACK<sup>TM</sup> modules are driven. Chapter 3.8 presents more general information how system consisting of 2ED300E17-SFO adapter board together with 2ED300C17-S EideDRIVER<sup>TM</sup> and MA300EXX can be practically utilized. Separated AN2007-06 describes MA300XX in details and gives practical hints on the topic.

Pin	Label	Function
X1.1, X1.6,		
X1.7, X1.13	n.c.	Not Connected
X1.14		
X1.2	IN B	PWM signal for channel B
X1.3	/FAULT	Fault detection output for combined for channel A and B
X1.4	IN A	PWM signal for channel A
X1.5	RESET	Reset signal for channel A and B
X1.8, X1.9	V <sub>DC</sub>	Primary voltage supply for DC/DC converter
X1.10, X1.11	GND	Primary ground for DC/DC converter and control singals
X1.12	Modus	Half-bridge or direct mode selection

Table 42ED300E17-SFO and the control signals for connector X1

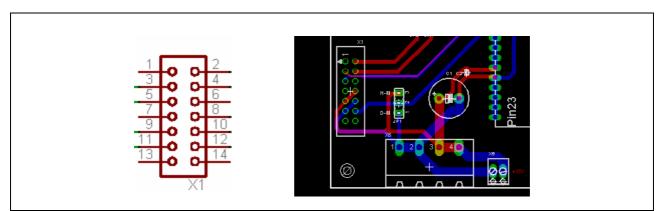


Figure 2 The 2ED300E17-SFO Evaluation Driver Board pin assignment for the driver control signals and DC/DC voltage power supply



## **Page Design features**

Table 5 Ad	able 5 Additional power supply of 2ED300E17-SFO (connector X5 and X6)				
Pin	Label	Function			
X5.1, X6.1, X6.2	GND	Primary ground for DC/DC converter			
X5.2, X6.3, X6.4	V <sub>DC</sub>	Primary voltage supply for DC/DC converter			

## Table 6 2ED300E17-SFO and connection to IGBT (connector X2)

Pin	Label	Function		
X2.1	V <sub>CE sat</sub> A	Desaturation voltage monitoring input – channel A		
X2.2	Gate A	Driver output to IGBT gate via an external gate resistor – channel A		
X2.3	COM A	Auxiliary emitter – channel A		
X2.4	Sense A	Control input for 'Shoft Shut Down' or 'Active Clamping' – channel A		
X2.5, X2.6, X2.7, X2.8, X2.9,	n.c.	Not Connected		
X2.10	V <sub>CE sat</sub> B	Desaturation voltage monitoring input – channel B		
X2.11	Gate B	river output to IGBT gate via an external gate resistor – channel B		
X2.12	COM B	Auxiliary emitter – channel B		
X2.13	Sense B	Control input for 'Shoft Shut Down' or 'Active Clamping' – channel B		

#### Table 7 2ED300E17-SFO and connection to MA300Exx

Pin	Label	Function		
X3.1, X7.1, X9.1	VA+	Isolated power supply, positive voltage – channel A (+15V)		
X3.2, X7.2, X9.2	СОМА	Auxiliary emitter – channel A		
X3.3, X7.3, X9.3	VA-	Isolated power supply, negative voltage – channel A (-15V)		
X3.4, X7.4, X9.4	Sense A	Gate - emitter signal source – channel A		
X3.5, X7.5, X9.5	V <sub>CE sat</sub> A	Desaturation voltage monitoring input – channel A		
X4.1, X8.1, X10.1	VB+	solated power supply, positive voltage – channel B (+15V)		
X4.2, X8.2, X10.2	СОМВ	uxiliary emitter – channel B		
X4.3, X8.3, X10.3	VB-	solated power supply, negative voltage – channel B (-15V)		
X4.4, X8.4, X10.4	Sense B	Gate – emitter signal source – channel B		
X4.5, X8.5, X10.5	V <sub>CE sat</sub> B	Desaturation voltage monitoring input – channel B		



Page Application Note

## 2.4 Mechanical dimensions of the 2ED300E17-SFO Evaluation Board

The 2ED300E17-SFO outline assembled with driver is shown in Figure 3.

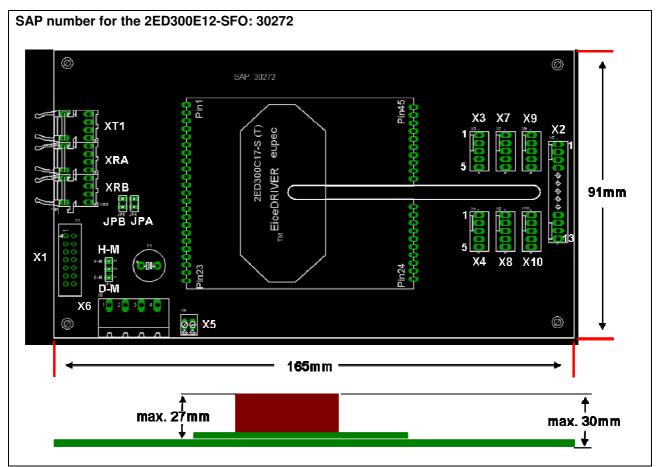


Figure 3 Dimensions of the 2ED300E17-SFO



Page Application Note

## 3 Application Note

The following chapter describes functionality of the 2ED300E17-SFO in combination with 2ED300C17-S /-ST EiceDRIVER™ in details.

## 3.1 **Power Supply**

The 2ED300E17-SFO provides +5V DC regulated voltage needed for fiber optic devices but also supplies the 2ED300C17-S /-ST EiceDRIVER<sup>™</sup>. In order to get the EiceDRIVER<sup>™</sup> properly working the external DC voltage source must fulfill requirements mentioned in chapter 2.3 and Table 1.

## 3.2 Input logic – PWM signals

The evaluation board offers two independend control interfaces: electrical and optical. The way of communication with the EiceDRIVER<sup>™</sup> can be selected by customer accordingly to the individual needs.

Electrical interface is simply activated by applying suitable signals<sup>1</sup> to appropriate pins in connector X1 as described in chapter 2.4, Table 4 and Table 5. Jumpers JPA and JPB visible on Figure 3 in that mode must be open.

When IGBT is driven using optical interface the fiber optic cables should be connected to receiver XRA in order to drive channel A and respectively XRB to drive channel B. Jumpers JPA and JPB in that case must be closed (Figure 3). No electrical signals except power supply connected to X1 are needed. Other connections should be removed. Keeping power supply connected to X5 or X6 and leaving X1 completelly unconnected seems to be the easiest solution.

## 3.3 Fault output and Reset

When the driver detects IGBT short circuit or  $V_{GE}$  drops bellow acceptable value the controlled IGBT will be switched off safetly and a fault will be reported. The event is additionally indicated by lighting diode D1. Voltage on X1.3 changes from  $V_{DC}$  level to around 1V and diode in transmitter XT1 is switched on.

Regardless PWM signals the IGBT stays off and fault is indicated. In order to get driver operating again the driver must be reseted in one of three possible ways:

- Pressing switch S1
- Apply voltage with a positive edge greater than 10V (max. V<sub>DC</sub>) to X1.5
- Keeping PWM signals on "low" level for more than 60ms

Keeping the switch S1 pressed long time may lead to permanent IGBT destruction when the reason for short circuit or low  $V_{GE}$  remains.

Reseting procedure is needed always after fault indication.

<sup>&</sup>lt;sup>1</sup> Detailed requirements for the electrical input interface are described in 2ED300C17-S /-ST datasheet available on <u>www.infineon.com</u> website.



## Page Application Note

## 3.4 Direct or Half-bridge mode selection

Two operation modes for the 2ED300C17-S EiceDRIVER™ are possible:

- Direct mode means that both channels A and B are working accordingly to PWM signals. It is possibile to switch on both channels A and B at the same time. This operation mode can be activated by setting the JP1 jumper on position marked as D-M (shorting pins 1 and 2 on Figure 3). When jumper JP1 is used there is no need to short X1.12 to GND of power supply
- Half-bridge mode is especially usefull when IGBTs are driven in half bridge configuration. By proper selection of capacitor values C4 and C5 the required dead time between channels A and B can be provided. This operation mode can be activated by setting the JP1 jumper on position marked as H-M (shorting pins 2 and 3 on Figure 3). When jumper JP1 is used there is no need to short X1.12 to V<sub>DC</sub>. Table 8 shows how dead time depends on these capacitors value. The dead time with not connected capacitors is 1,6µs.

#### Table 8Dead time settings

C4 and C5	n.c.	47pF	100pF	220pF	330pF	470pF	1nF
Dead time	1.6µs	2µs	2,4µs	3,4µs	4,3µs	5,4µs	9,6µs

The 2ED300E17-SFO is already equipped with C4=C5=470pF meaning that when JP1 is on position H-M than interlocking time between channel A and B will reach  $5,4\mu$ s.

## 3.5 SSD – 'Soft Shut Down'

The 'Soft Shut Down' function secures an IGBT module when short circuit current is being switched off. This function is widely described in 2ED300C17-S EiceDRIVER<sup>TM</sup> application note (chapter 3.8). Resistor called  $R_{SSD}$  in the 2ED300E17-SFO is called R3, R31 (are in parallel) for channel A and R4, R41 (are in parallel) for channel B and should be selected accordingly to module type.

These resistors originally are not soldered. In order to provide the correct SSD function resistors R3, R31, R4 and R41 must be properly calculated. The calculation example is shown bellow:

$$\frac{R_{SSD}}{k\Omega} = \frac{346.8}{\frac{Q_q \cdot 16.8}{\mu C} - 51}$$
(1)

where:

Qg - gate charge of selected IGBT module type

Due to resistors parallel connection the final value gives formula 3.

$$R3 = R31 = R4 = R41 = 2 \cdot R_{SSD}$$
(2)

When PrimePACK<sup>™</sup> modules are used than Table 9 shows already calculated R<sub>SSD</sub> resistors values.

i abio o i i isso ookii igo	
Module type	R3, R31, R4, R41 (1206 package) proposed values
FF650R17IE4	10 kΩ
FF1000R17IE4	5,6 kΩ
FF600R12IP4 / FF600R12IE4	22 kΩ
FF900R12IP4 / FF900R12IP4D	8k2 kΩ
FF1400R12IP4	4k7 kΩ

#### Table 9 R<sub>SSD</sub> settings



## Page Application Note

## 3.6 Reference curve and and trigger suppression

Correct short circuit operation requires also proper short circuit detection. The issue has been described in 2ED300C17-S EiceDRIVER™ in chapter 3.7.

Passive components like  $C_{SA}$ ,  $R_{SA}$ ,  $C_{SB}$ ,  $R_{SB}$  are responsible for suitable 'blanking time' and set up the  $V_{CE}$  desaturation threshold voltage. In 2ED300E17-SFO adapter board these passive components are respectively named as C12, R7 - channel A and C13, R8 – channel B.

Additional ones responsible for trigger suppression are  $C_{VCE}$  and  $R_{VCE}$  and their equivalents in 2ED300E17-SFO are C10, R5 – channel A and C11, R6 – channel B.

All components mentioned in this chapter are soldered into 2ED300E17-SFO and their values as default are listed bellow:

C12=C13= 560pF

R7=R8= 22kΩ


C10=C11=1nF

R5=R6=470Ω

It has to be noticed that those values may not be proper for all IGBT modules driven by this adapter board.
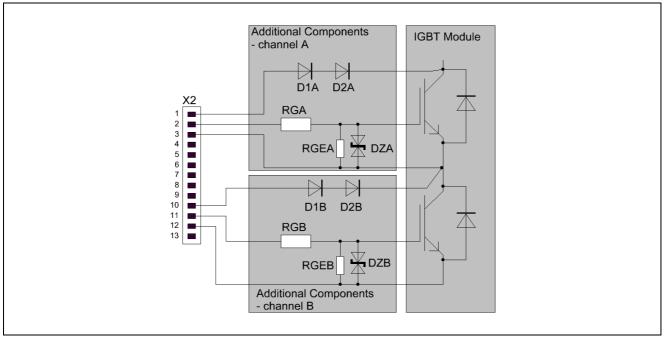
## 3.7 The minimum circuit for proper X2 utilisation

The 2ED300E17-SFO evaluation board together with 2ED300C17-S EiceDRIVER<sup>™</sup> makes system able to drive various Infineon IGBT modules. Connector X2 provides needed functions nevertheless basic circuit shown on Figure 4 is required.



#### Figure 4 Additional components needed for driving IGBT module

Practical selection for parts visible on Figure 4 is described in 2ED300C17-S EiceDRIVER™ application note chapter 3.6.



#### Page Schematic, Layout and Bill of Material

## 3.8 Operation with MA300E12 or MA300E17

As mentioned in introduction of this application note the 2ED300E17-S evaluation board is prepared for easy usage together with MA300Exx. To operate the MA300Exx it should be screwed to the PrimePACK<sup>™</sup> module and connected by simple cable to one pair of 2ED300E17-SFO connectors e.g. X9 and X11. Parallel IGBT module operation is also possible and maximum number of them in configuration presented on Figure 5 is three. Additional aluminium capacitors with minimum value of 100µF/35V connected in parallel across C30, C35 and C40, C45 for module proper operation is required.

Table 9 presents resistors value needed for correct short circuit protection. When parallel module operation is intended those resistors values must be recalculated accordingly to exaplme given in chapter 3.5.

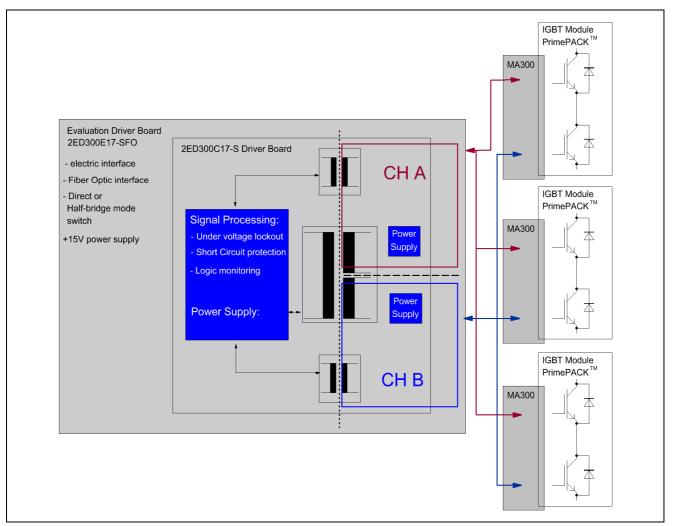


Figure 5 Driver set for parallel PrimePACK™ IGBT module operation



## Page Schematic, Layout and Bill of Material

## 4 Schematic, Layout and Bill of Material

To meet the individual customer requirement and make the evaluation board useful for development or modification, all necessary technical data like schematic, layout and components are included in this chapter.

## 4.1 Schematic



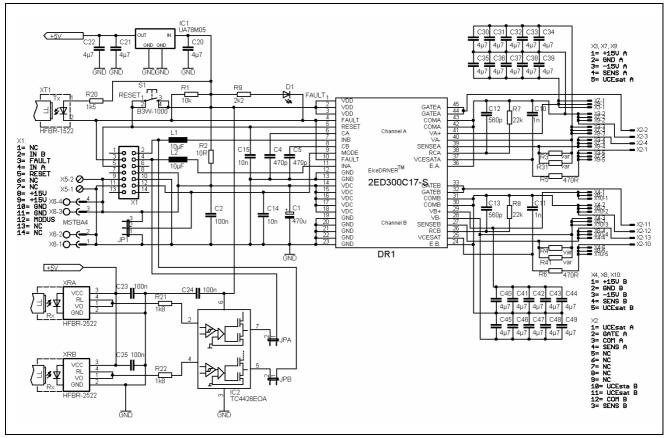


Figure 6 The 2ED300E17-SFO schematic

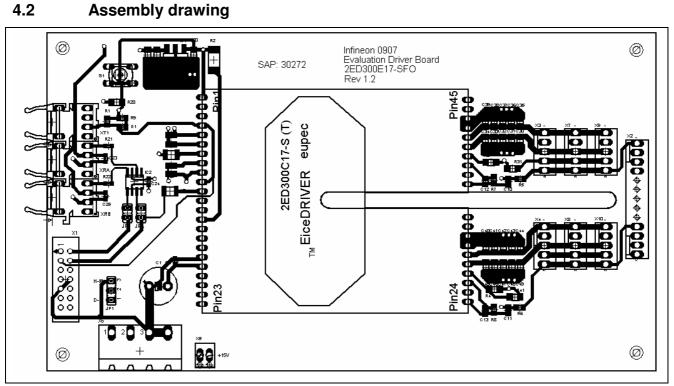
 
## Page Schematic, Layout and Bill of Material





## 4.3 Layout

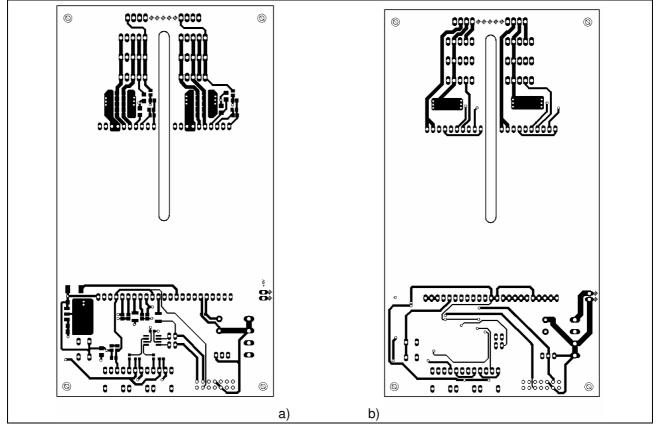


Figure 8 2ED300E17-SFO adapter board – a) Top layer and b) Layer 2



#### Page Schematic, Layout and Bill of Material

## 4.4 Bill of Material

The bill of material not only includes a part list, but also assembly notes.

The tolerances for resistors should be less or equal  $\pm 1$  %, for capacitors of the type C0G less or equal  $\pm 5$  % and for capacitors of the type X7R less or equal  $\pm 10$  %.

#### Table 10 Bill of Material for 2ED300E17-SFO adapter board

Туре	Value / Type	Package EIA	QTY	Name Part	Recommended Manufacturer	Assembly
Resistor	variable	1206	4	R3, R4, R31, R41	no special	no
Resistor	10k	0805	1	R1	no special	yes
Resistor	10R	2512	1	R2	no special	yes
Resistor	470	0805	2	R5, R6	no special	yes
Resistor	22k	0805	2	R7, R8	no special	yes
Resistor	2k2	0805	1	R9	no special	yes
Resistor	1k5	1206	1	R20	no special	yes
Resistor	1k8	0605	2	R21, R22	no special	yes
Capacitor	470p/50V/CO G	0805	2	C4, C5	no special	yes
Capacitor	560p/50V/CO G	0805	2	C12, C13	no special	yes
Capacitor	1n/50V/COG	0805	2	C10, C11	no special	yes
Capacitor	10n/50V/X7R	0805	2	C14, C15	no special	yes
Capacitor	100n/50V7R X	0805	4	C2, C23, C24, C25	no special	yes
Capacitor	4µ7/25V/X7R	1206	23	C20, C21, C22, C30, C31, C32, C33, C34, C35, C36, C37, C38, C39, C40, C41, C42, C43, C44, C45, C46, C47, C48, C49	Murata	yes
Capacitor	470µ/35V	CPOL- EUE-10.5	4	C1	no special	yes
Inductor	10µH	1210	2	L1, L2	Murata	yes
Semiconductor	TC4426EOA	SO8	1	IC2	Microchip	yes
Semiconductor	UA78M05CD CYG3	SOT223	1	IC1	no special	yes
Semiconductor	HFBR-2522Z		2	XRA, XRB	AVAGO	no
Semiconductor	HFBR-1521Z		1	XT1	AVAGO	no
Semiconductor	LED	0805	1	D1		yes
Jumper	3-pol	JP2	2	JPA, JPB		yes
Jumper	2-pol	JP1	1	JP1		yes
Connector	6-64 /14 pole		1	X1	Harting	yes
Connector	13-pol		1	X2	Moelex	no
Connector	6410-5A		2	X3, X4	Moelex	yes
Connector	6410-5A		4	X7, X8, X9, X10	Moelex	yes
Connector	MPT 05/2 2,54mm	2POL2.5 4	1	X5	Phoenix	yes
Connector	MSTBA 2.5/4-G-5.08		1	X6	Phoenix	no
Switch	B3W-1000	B3W- 1000	1	S1	Omron	yes
Driver	2ED300C17- S		1	DR1	Infineon	no



## Page How to order Evaluation Driver Boards

## 5 How to order Evaluation Driver Boards

Every Evaluation Driver Board has its own number and can be ordered via your Infineon Sales Partner. Information can also be found at the Infineons Web Page: <u>www.infineon.com</u>

CAD-data for the board decribed here are available on request. The use of this data is subjected to the disclaimer given in this AN. Please contact: <u>IGBT.Application@infineon.com</u>

IFX order number for 2ED300E17-SFO: 30272

Please remember to order driver separately: IFX order number for 2ED300C17-S: 29831 IFX order number for 2ED300C17-ST: 29832

http://www.infineon.com

## **X-ON Electronics**

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Power Management IC Development Tools category:

Click to view products by Infineon manufacturer:

Other Similar products are found below :

EVB-EP5348UI MIC23451-AAAYFL EV MIC5281YMME EV 124352-HMC860LP3E DA9063-EVAL ADP122-3.3-EVALZ ADP130-0.8-EVALZ ADP130-1.8-EVALZ ADP1740-1.5-EVALZ ADP1870-0.3-EVALZ ADP1874-0.3-EVALZ ADP199CB-EVALZ ADP2102-1.25-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP2102-3-EVALZ ADP2102-4-EVALZ AS3606-DB BQ25010EVM BQ3055EVM ISLUSBI2CKIT1Z LM2734YEVAL LP38512TS-1.8EV EVAL-ADM1186-1MBZ EVAL-ADM1186-2MBZ ADP122UJZ-REDYKIT ADP166Z-REDYKIT ADP170-1.8-EVALZ ADP171-EVALZ ADP1853-EVALZ ADP1873-0.3-EVALZ ADP198CP-EVALZ ADP2102-1.0-EVALZ ADP2102-1-EVALZ ADP2107-1.8-EVALZ ADP1853-EVALZ ADP1873-0.3-EVALZ ADP198CP-EVALZ ADP2102-1.0-EVALZ ADP2102-1-EVALZ ADP2107-1.8-EVALZ ADP5020CP-EVALZ CC-ACC-DBMX-51 ATPL230A-EK MIC23250-S4YMT EV MIC26603YJL EV MIC33050-SYHL EV TPS60100EVM-131 TPS65010EVM-230 TPS71933-28EVM-213 TPS72728YFFEVM-407 TPS79318YEQEVM UCC28810EVM-002 XILINXPWR-083 LMR22007YMINI-EVM