

# TC1793

## AP32163

Design Guideline for TC1793 Microcontroller Board Layout

Application Note V1.2 2012-02

Microcontrollers

Edition 2012-02 Published by Infineon Technologies AG 81726 Munich, Germany © 2012 Infineon Technologies AG All Rights Reserved.

#### LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

#### Information

For further information on technology, delivery terms and conditions and prices, please contact the nearest Infineon Technologies Office (www.infineon.com).

#### Warnings

Due to technical requirements, components may contain dangerous substances. For information on the types in question, please contact the nearest Infineon Technologies Office.

Infineon Technologies components may be used in life-support devices or systems only with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.



Device1					
Revision History: V1.2, 2012-02 Previous Version: V1.1, 2011-11					
10	Fig-4 changed.				

We Listen to Your Comments	
Is there any information in this document that you feel is wrong, unclear or missing?	
Your feedback will help us to continuously improve the quality of this document.	
Please send your proposal (including a reference to this document) to:	$\bigtriangledown$
mcdocu.comments@infineon.com	



### **Table of Contents**

## **Table of Contents**

1	Overview	5
1.1	General Information	
1.2	Pinout of TC1793	5
2	PCB Design Recommendations	5
<b>2</b> 2.1	PCB Design Recommendations	



## 1 Overview

The TC1793 is a 32-Bit microcontroller in a BGA-416 package, which requires a PCB carefully designed for electromagnetic compatibility. In addition to the Infineon PCB Design Guidelines for Microcontrollers (AP24026), which gives general design rule informations for PCB design, some product-specific recommendations and guidelines for the TC1793 are discussed here.

## 1.1 General Information

The microcontroller has four supply domains ((VDD=1.3V for Core, VDDP=3.3V for I/O Pad, VDDEBU=2.5V-3.3V for EBU, VDDM=3.3V or 5V for ADC), which should be decoupled individually.

The power supply feeding from the regulator outputs to each domain can be made on a supply layer (POWER).

## 1.2 Pinout of TC1793

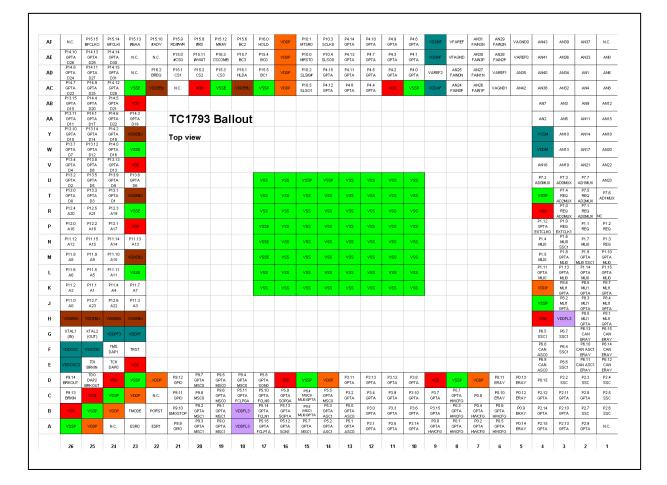


Figure 1 Pinout of TC1793 (BGA-416):

## 2 PCB Design Recommendations

- To minimize the EMI radiation on the PCB the following signals have to be considered as critical:
  - BFCLKOUT: EBU clock output
  - LVDS Pins
  - MLI Pins
  - MSC Pins



- ERAY Pins
- Supply Pins

Route these signals with adjacent ground reference and avoid signal and reference layer changes. Route them as short as possible.

Routing ground on each side can help to reduce coupling to other signals.


For unused <u>"Output, Supply, Input and I/O "</u> pins following points must be considered:

1. Supply Pins (Modules)	See the User's Manual.
2. I/O-Pins	• Should be configured as output and driven to static low in the weakest driver mode in order to improve EMI behaviour. Confuguration of the I/O as input with pullup is also possible.
	<ul> <li>Solderpad should be left open and not be connected to any other net (layout isolated PCB-pad only for soldering).</li> </ul>
3. Output Pins including LVDS	Should be driven static in the weakest driver mode.
	<ul> <li>If static output level is not possible, the output driver should be disabled.</li> </ul>
	<ul> <li>Solderpad should be left open and not be connected to any other net (layout isolated PCB-pad only for soldering).</li> </ul>
4.Input Pins without internal pull device	<ul> <li>For pins with alternate function see product target specification to define the necessary logic level.</li> </ul>
	<ul> <li>Should be connected with high-ohmic resistor to GND (range 10k – 1Meg) wherever possible. No impact on design is however expected if a direct connection to GND is made.</li> </ul>
	<ul> <li>Groups of 8 pins can be used to reduce number of external pull-up/down devices (keep in mind leakage current).</li> </ul>
5. Input Pins with internal pull device	For pins with alternate function see product specification to define the necessary logic level
	<ul> <li>Should be configured as pull-down and should be activated static low (exception: if the User's Manual requires high level for alternate functions). No impact on design is expected if static high level is activated.</li> </ul>
	<ul> <li>Solderpad should not be connected to any other net (isolated PCB-pad only for soldering)</li> </ul>

- The ground system must be designed as follows:
  - Separate analog and digital grounds.
  - The analog ground must be separated into two groups:
    - 1. Ground for OSC and PLL (VSSOSC for VDDOSC, VDDOSC3, VDDPF and VDDPF3) as common star point.
    - 2. Ground for ADC (VSSM for VDDM, VSSMF for VDDMF/VDDAF) as common star point.
- To reduce the radiation / coupling from the oscillator circuit, a separated ground island on the GND layer should be made. This ground island can be connected at one point to the GND layer. This helps to keep noise generated by the oscillator circuit locally on this separated island. The ground connections of the load capacitors and VSSOSC should also be connected to this island. Traces for the load capacitors and Xtal should be as short as possible.



- The power distribution from the regulator to each power plane should be made over filters (see Figure 2).
- RC Filters can be inserted in the supply paths at the regulator output and at the branchings to other module supply pins like VDDOSC, VDDOSC3, VDDFL3, VDDPF, VDDPF3, VDDM, VDDMF, VDDAF (see Figure 2). Using inductance or ferrite beads (5 10 µH) instead of the resistors can improve the EME behaviour of the circuit and reduce the radiation up to ~10dBµV on the related supply net.
- OCDS must be disabled.
- Select weakest possible driver strengths and slew rates for all I/Os (see Scalable Pads AppNote AP32111).
- Use lowest possible frequency for SYSCLK.
- Avoid cutting the GND plane by via groups. A solid GND plane must be designed.

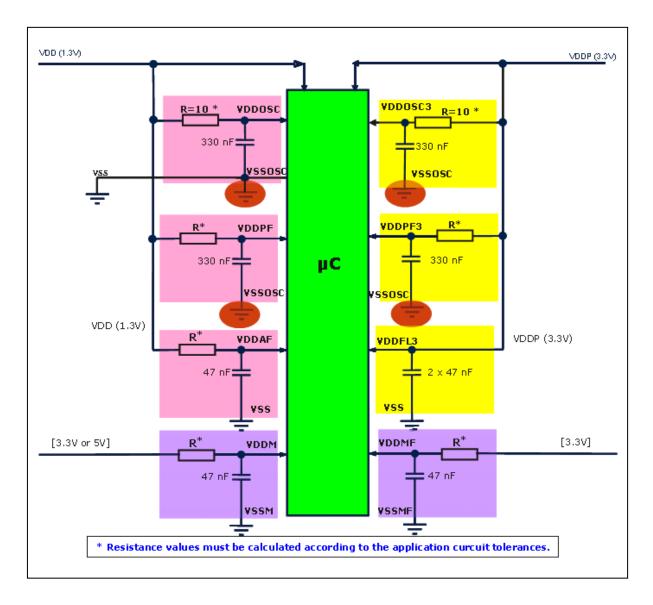

## Figure 2 Filtering of VDDOSC, VDDOSC3, VDDFL3, VDDPF, VDDPF3, VDDM, VDDMF, VDDAF supply pins



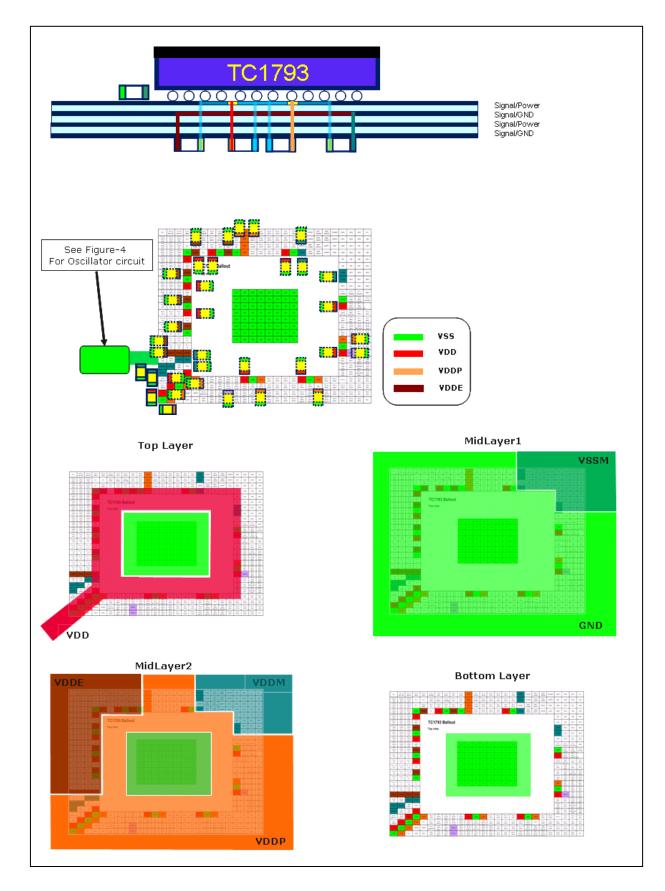
### 2.1 Decoupling

- The three supply domains VDD, VDDP and VDDEBU of TC1793 should be decoupled separately (see decoupling placement example in Figure 3).
- Type of capacitors:
  - Values: 47 nF, 100 nF, 330 nF
  - X7R Ceramic Multilayer (low ESR and low ESL)
- All supply pins should be connected first to the dedicated decoupling capacitor and then from the capacitors over vias to the power planes.
- All VSS pins should be connected to the GND.
- The decoupling capacitors should be placed directly under the IC or if necessary, some capacitors can be placed on top layer close to the supply pins of the IC.
- Ground plane on bottom layer can be used to connect the capacitors. If no plane is used, they should be connected with vias to the GND layer.
- Multiple vias should be used at capacitors to get a low impedance connection between capacitors and POWER/GND planes or pins.
- All capacitors must be placed as close as possible to the related supply pin group.

In Figure 3 shown examples are based on device power supply concept and implementation. Alternative implementations are also acceptable and must be evaluated within application by customer.





### Figure 3 Capacitor Placement Example for Decoupling of TC1793 (BGA-416) on a four layer board



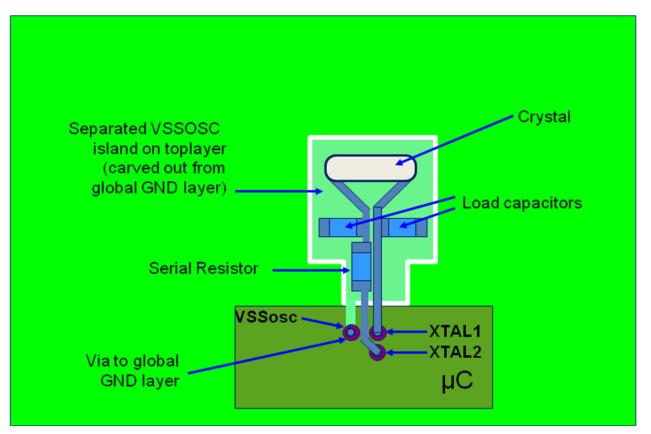


Figure 4 Layout Proposal Oscillator Circuit



Capacitor	Supply	Pins(BGA-416)
47 nF	VDD	B26 / C25
47 nF	VDD	D24 / E23
47 nF	VDD	D16
47 nF	VDD	D9
47 nF	VDD	H4
47 nF	VDD	R4
47 nF	VDD	AC11
47 nF	VDD	AC20
47 nF	VDD	AB23
47 nF	VDD	Y23
47 nF	VDD	P23
47 nF	VDDP	A25 / B24
47 nF	VDDP	C23 / D22
47 nF	VDDP	D14
47 nF	VDDP	D7
47 nF	VDDP	K4
47 nF	VDDP	AC16 / AD16
47 nF	VDDP	AE16 / AF16
47 nF	VDDE	H26 / H25
47 nF	VDDE	H24 / H23
47 nF	VDDE	M23
47 nF	VDDE	T23
47 nF	VDDE	Y23
47 nF	VDDE	AC22
47 nF	VDDE	AC18
330 nF	VDDOSC	F26
330 nF	VDDOSC3	E26
47 nF	VDDFL3	H3
47 nF	VDDFL3	A18 / B18
330 nF	VDDPF	G23
330 nF	VDDPF3	G24
47 nF	VDDM	W4
47 nF	VDDMF	AE9
47 nF	VDDAF	AC9

## 2.2 Decoupling Capacitor List:

<u>Note:</u> This application note contains design recommendations from Infineon Technologies point of view. Effectiveness and performance of the final application implementation must be validated by customer, based on dedicated implementation choices.

www.infineon.com

Published by Infineon Technologies AG

## **X-ON Electronics**

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Development Boards & Kits - Other Processors category:

Click to view products by Infineon manufacturer:

Other Similar products are found below :

EVB-MEC1418MECC 20-101-1252 CC-ACC-18M433 STM8S/32-D/RAIS RTK0EN0001D01001BZ MAXQ622-KIT# YR0K50571MS000BE QB-R5F104PJ-TB CC-ACC-ETHMX OV-7604-C7-EVALUATION-BOARD SK-AD02-D62Q1747TB SK-BS01-D62Q1577TB ST7MDT1-EMU2 GROVE BASE KIT FOR RASPBERRY PI CY8CKIT-143A RASPBERRY PI PICO EK-MPC5744P KITAURIXTC234TFTTOBO1 ENW89854AXKF ENWF9201AVEF QB-R5F104LE-TB LV18F V6 64-80-PIN TQFP MCU CARD EMPTY LV-24-33 V6 44-PIN TQFP MCU CARD EMPTY LV-24-33 V6 64-PIN TQFP MCU CARD EMPTY LV-24-33 V6 80-PIN TQFP 1 MCU CARD EMPTY 32X32 RGB LED MATRIX PANEL - 6MM PITCH 3.3 - 5 VTRANSLATOR READY FOR XMEGA CASING (WHITE) RELAY4 BOARD ETHERNET CONNECTOR RFID CARD 125KHZ - TAG RFID READER RFM12B-DEMO MAROON 3G CLICK (FOR EUROPE AND AUSTRALIA) MAX232 MAX3232 BOARD ARTY S7-50 TINKERKIT HALL SENSOR TOUCHPANEL TOUCHPANEL CONTROLLER MIKROBOARD FOR AVR WITH ATMEGA128 MIKROBOARD FOR PSOC WITH CY8C27643 MIKROBUS CAPE MIKRODRIVE MIKROETH 100 BOARD MIKROLAB FOR 8051 L MIKROPROG TO ST-LINK V2 ADAPTER BANANA PI GPIO EXTEND MODULE BATTERY BOOST SHIELD BOARD