

# ZL9101EVAL1Z

Digital DC/DC 12A Module Evaluation Board

AN1625 Rev 0.00 February 4, 2011

# **Description**

The ZL9101M is a 12A variable output, step-down power supply module. Included in the module is a high-performance digital PWM controller, power MOSFETs, an inductor, and all the passive components required for a complete DC/DC power solution. The ZL9101M operates over a wide input voltage range and supports an output voltage range of 0.6V to 4V, which can be set by external resistors or via the PMBus. This high-efficiency power module is capable of delivering 12A. Only bulk input and output capacitors are needed to finish the design. The output voltage can be precisely regulated to as low as 0.6V with  $\pm 1\%$  output voltage regulation.

The ZL9101EVAL1Z is a 6-layer board that provides a single-phase power rail up to 12A loads. The board is designed to efficiently transfer heat away from the module with passive cooling.

A USB to SMBus adapter is used to connect the ZL9101EVAL1Z board to a PC. The PMBus command set is accessed by using the PowerNavigator  $^{\text{TM}}$  evaluation software.

## **Key Features**

- · Complete Switch Mode Power Supply
- 12A DC Output Current
- Adjustable +0.6V to +4V Output Range
- Up to 90% Efficiency
- Digital Control PWM
- Fixed 615kHz Switching Frequency
- · Fast Transient Response
- Enable Function Option
- · Power-Good Indicator
- Convenient Power Connection
- . Multiple Power Options
- Single Supply Operation
- . Configurable Through SMBus

# **Key Specifications**

The ZL9101EVAL1Z has been designed and optimized for the following parameters:

- V<sub>IN</sub> = 12V
- V<sub>OUT</sub> = 1.2V
- I<sub>OUT(MAX)</sub> = 15A
- F<sub>SW</sub> = 615kHz
- V<sub>OUT(RIPPLE)</sub> < 1%</li>
- Transient Response = 3% (3A to 9A step at 2.5V/μs)

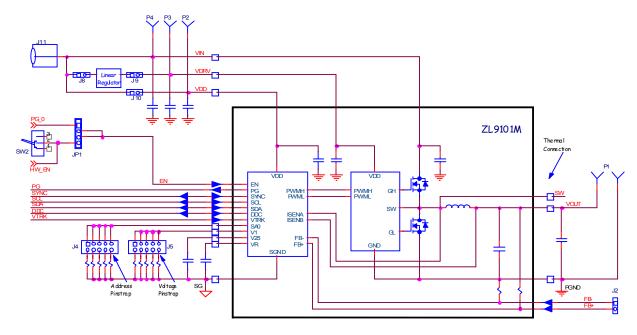


FIGURE 1. ZL9101EVAL1Z EVALUATION BOARD BLOCK DIAGRAM

# **Functional Description**

The ZL9101EVAL1Z evaluation board provides all the circuitry required to evaluate the features of the ZL9101M module. The ZL9101EVAL1Z has a performance-optimized, single-phase ZL9101M circuit layout that allows operation up to the maximum rated output current. Power options and load connections are provided through plug-in sockets and shorting jumpers.

Figure 1 shows a functional block diagram of the ZL9101EVAL1Z board. The SMBus address is selectable through J4 located on the top side of the board. All power to the board ( $V_{IN}$  and  $I^2C$  bus) must be removed before changing the jumpers.

The hardware enable function is controlled by a toggle switch on the ZL9101EVAL1Z board. The power-good (PG) LED indicates the state of PG when external power is applied to the ZL9101EVAL1Z board. The right-angle headers at opposite ends of the board are for connecting a USB to an SMBus adapter board or for daisy-chaining of multiple evaluation boards.

Figure 2 shows the ZL9101EVAL1Z operational circuit. The circuit consists of the ZL9101M module and supporting components.

Figure 3 shows the ZL9101EVAL1Z interface schematic.

Figures 4 through 9 show the layers of the ZL9101EVAL1Z evaluation board.

## **Basic Operation**

The ZL9101EVAL1Z evaluation board is easy to set up and operate. It is optimally configured, out of the box, to provide 1.2V at 12A from a 12V source. All input and output connections should be made before applying power.

The ZL9101M module requires a configuration file in order to operate. The ZL9101M supports pinstrap configuration for output voltage and SMBus address. All other parameters must be configured with a text-based configuration file. See application note AN2031 for more information on writing configuration files. An example configuration file is listed at the end of this document.

## **Pinstraps**

The ZL9101M requires a configuration file for normal operation; however, there are two pinstrap functions to be configured: Voltage and SMBus address. Ensure that input power is removed, and then set the address and voltage pinstraps using J4 and J6. Apply  $V_{DD}$  power, and the new settings will be in effect.

#### **PMBus Operation**

The ZL9101M utilizes the PMBus protocol. The PMBus functionality can be controlled via USB from a PC running the PowerNavigator  $^{\text{TM}}$  evaluation software in a Windows XP or Windows 2000/NT operating system.

Install the PowerNavigator<sup>™</sup> software using the CD included in the ZL9101EVAL1Z kit. For PMBus operation, connect the USB-to-SMBus dongle board to J7 of the ZL9101EVAL1Z board. Connect the desired load and an appropriate power supply to the input. Place the ENABLE switch in "DISABLE" and turn on the power. The PowerNavigator <sup>™</sup> evaluation software allows modification of all ZL9101M PMBus parameters. See Application Note AN2033 for PMBus command details. Use the mouse-over pop-ups for PowerNavigator <sup>™</sup> help. Manually configure the ZL9101M through

PowerNavigator  $^{\text{TM}}$  or load a predefined scenario from a configuration file.

The ENABLE switch can then be moved to "ENABLE" and the ZL9101M can be tested. Alternately, the PMBus ONOFF, CONFIG, and OPERATION commands can be used.

### **Single-Supply Operation**

The ZL9101EVAL1Z board was designed to facilitate operation from a single power supply input. The single input power mode reduces the number of connections but results in a minor reduction of efficiency.

The driver bias is supplied by an onboard linear regulator. Figure 3 shows the onboard regulator circuit for powering the ZL9101M driver. Jumpers J8 and J9 connect the supply power to the linear regulator that is used to power the driver, and J6 connects input power to the ZL9101M digital module. If single-supply operation is desired, J6, J8, and J9 must be installed.

# Multi-Supply Operation (External Driver Supply)

To operate the ZL9101EVAL1Z driver from an external power supply, remove J8 and J9, and connect an external power supply to the driver connector, P3, between 4.5V to 6.5V.

To operate the ZL9101EVAL1Z board using different power supplies for the controller and FETs, remove J6 and apply an external power supply to power the FETs to P4 to between 3.0V and 14V.

Apply a power supply voltage to the ZL9101M module through the P2 connector.

If the V<sub>DD</sub> voltage is  $4.5V \le V_{DD} \le 5.5V$ , then apply 4.5V to 5.5V to P2, and connect V<sub>R</sub> to V<sub>DD</sub>. Do not exceed 5.5V while V<sub>R</sub> is connected to V<sub>DD</sub> or permanent damage will result.

If the  $V_{DD}$  voltage is  $5.5V \le V_{DD} \le 14V$ , then apply 5.5V to 14V to P2, and do not connect to  $V_R$ .

The ZL9101EVAL1Z comes configured to use hardware Enable. Toggle the power switch to the Enable position to power on. Use the GUI to change the configuration, if desired.

#### **Power Good**

The ZL9101M provides a Power-Good (PG) signal, which indicates that the output voltage is within a specified tolerance of its target level and that no fault condition exists. By default, the PG pin asserts if the output is within 10% of the target voltage. These limits and the polarity of the pin may be changed via the I<sup>2</sup>C/SMBus interface. See Application Note AN2033 for details.

A PG delay period is defined as the time from when all conditions within the ZL9101M for asserting PG are met to when the PG pin is actually asserted. This feature is commonly used instead of using an external reset controller to control external digital logic. By default, the ZL9101M PG delay is set equal to the soft-start ramp time setting of 10ms. The PG delay may be set independently of the soft-start ramp by using the I<sup>2</sup>C/SMBus as described in Application Note AN2033.



## **Switching Frequency and PLL**

The ZL9101M incorporates an internal phase-locked loop (PLL) to clock the internal circuitry. The PLL can be driven by an external clock source connected to the SYNC pin via J7 or J14. When using the internal oscillator, the SYNC pin can be configured as a clock source.

The internal switching frequency of the ZL9101M is 615kHz. Operation below 615kHz will increase the inductor ripple current and cause permanent damage.

### **Loop Compensation**

The ZL9101M operates as a voltage-mode synchronous buck controller with a fixed frequency PWM scheme. The module is internally compensated via the  $I^2C/SMBus$  interface. The PID settings are included in the configuration file stored on the ZL9101M; the settings are shown in "Default Configuration File" on page 6 for reference. The compensation tool, CompZL  $^{\text{TM}}$  can be used to generate appropriate PID settings for other circuit configurations.

## **Adaptive Diode Emulation**

Adaptive diode emulation mode turns off the low-side FET gate drive at low load currents to prevent the inductor current from going negative, thus reducing energy losses and increasing overall efficiency. Diode emulation is available to single-phase devices only.

NOTE: The overall bandwidth of the device may be reduced when in diode emulation mode. It is recommended that diode emulation be disabled prior to applying significant load steps.

## **Input Undervoltage Lockout**

The input undervoltage lockout (UVLO) prevents the ZL9101M from operating when the input falls below a preset threshold, indicating the input supply is out of its specified range. The UVLO threshold (V $_{\rm UVLO}$ ) can be set between 2.85V and 16V using the  $\rm I^2C/SMBus$  interface.

Once an input undervoltage fault condition occurs, the device can respond in a number of ways as follows:

- 1. Continue operating without interruption.
- Continue operating for a given delay period, followed by shutdown if the fault still exists. The device remains in shutdown until instructed to restart.

#### **Connectors and Jumpers**

Connector and jumpers are shown in Figure 10.



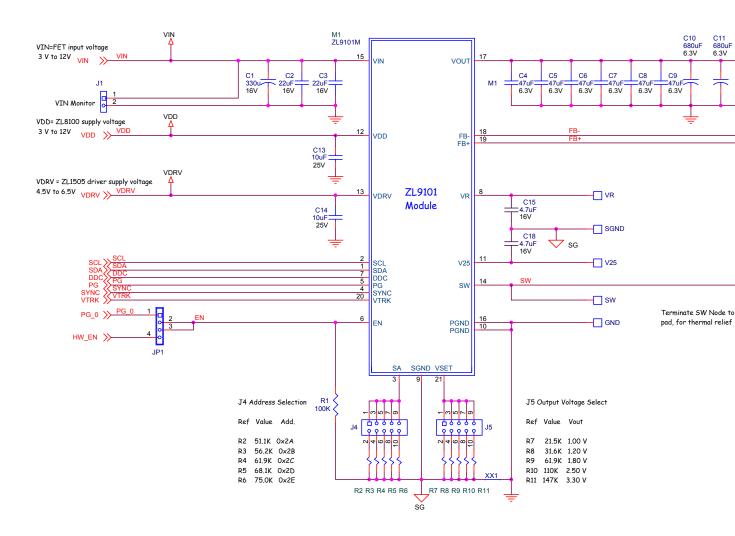


FIGURE 2. ZL9101EVAL1Z CIRCUIT SCHEMATIC

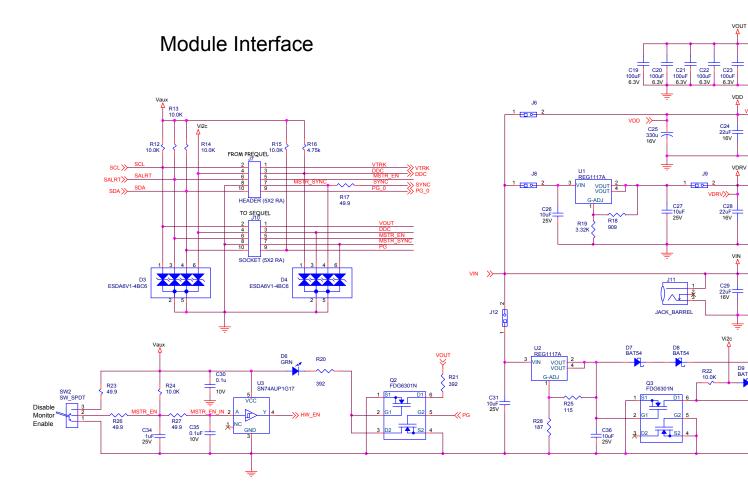


FIGURE 3. ZL9101EVAL1Z INTERFACE SCHEMATIC

# **Default Configuration File**

The following text is loaded into the ZL9101M devices on the ZL9101EVAL1Z evaluation board as the default settings. This configuration file can be loaded using the PowerNavigator™ software, ConfigCheck™ software, or a user-created application. The # symbol denotes a comment line.

- # Intersil ZL9101M 12/20/2010
- # ZL Configuration File Revision 2
- # Schematic revision level
- # BOM revision level
- # ZL Author
- # Change log:

RESTORE\_FACTORY
STORE\_DEFAULT\_ALL
STORE\_USER\_ALL
RESTORE\_DEFAULT\_ALL

MFR\_ID Intersil

MFR\_MODEL ZL9101EVAL1Z

MFR\_REVISION REV\_2.0 MFR\_LOCATION Austin

 MFR\_DATE
 12\_20\_2010

 MFR\_SERIAL
 1p2V\_15A

 ON\_OFF\_CONFIG
 0x1A

#VOUT\_COMMAND

#VOUT\_OV\_FAULT\_LIMIT

- - - - - -

**#VOUT\_MAX** 

#VOUT\_UV\_FAULT\_LIMIT #VOUT\_MARGIN\_HIGH #VOUT\_MARGIN\_LOW

#VOUT\_DROOP

IOUT\_SCALE

#POWER\_GOOD\_ON 5
#POWER\_GOOD\_DELAY 5

1.556

 IOUT\_CAL\_OFFSET
 -2.30

 TON\_DELAY
 5

 TON\_RISE
 5

 TOFF\_DELAY
 5

 TOFF\_FALL
 5

 FREQUENCY\_SWITCH
 615

 VOUT\_OV\_FAULT\_RESPONSE
 0x80

VOUT\_UV\_FAULT\_RESPONSE 0x80

OVUV\_CONFIG 0x80

IOUT\_OC\_FAULT\_LIMIT 25

IOUT\_AVG\_OC\_FAULT\_LIMIT 25

-20 IOUT\_UC\_FAULT\_LIMIT -20 IOUT\_AVG\_UC\_FAULT\_LIMIT 0x80 MFR\_IOUT\_OC\_FAULT\_RESPONSE MFR\_IOUT\_UC\_FAULT\_RESPONSE 0x80 7.0 MFR\_VMON\_OV\_FAULT\_LIMIT 0x80 VMON\_OV\_FAULT\_RESPONSE 4.5 MFR\_VMON\_UV\_FAULT\_LIMIT 0x80 VMON\_UV\_FAULT\_RESPONSE 14.3 VIN\_OV\_WARN\_LIMIT 14.5 VIN\_OV\_FAULT\_LIMIT 0x80 VIN\_OV\_FAULT\_RESPONSE 4.2 VIN\_UV\_WARN\_LIMIT 4.0 VIN\_UV\_FAULT\_LIMIT 0x80 VIN\_UV\_FAULT\_RESPONSE 110.0 OT\_WARN\_LIMIT 125 OT\_FAULT\_LIMIT 0x80 OT\_FAULT\_RESPONSE -20 UT\_WARN\_LIMIT -40 UT\_FAULT\_LIMIT 0x00 UT\_FAULT\_RESPONSE

PID\_TAPS A=16133.25, B=-27119.00, C=10998.50

DEADTIME 0x3838
DEADTIME\_CONFIG 0x8C06
DEADTIME\_MAX 0x2828
MAX\_DUTY 92

**#TRACK\_CONFIG** 

1.0 **#XTEMP\_SCALE** 10.0 **#XTEMP\_OFFSET** 0x8311 MFR\_CONFIG 0x00000000 NLR\_CONFIG 0x0031 USER\_CONFIG 0x28 TEMPCO\_CONFIG 0x8880 MISC\_CONFIG 0x0000 ISHARE\_CONFIG 0x0000 **INTERLEAVE** 0x0000 **SEQUENCE** 0x0000000 DDC\_GROUP 0x0000 DDC\_CONFIG 0.30 **INDUCTOR** 

STORE\_DEFAULT\_ALL
RESTORE\_DEFAULT\_ALL



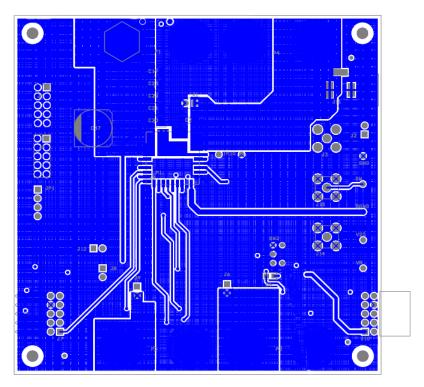


FIGURE 4. TOP LAYER

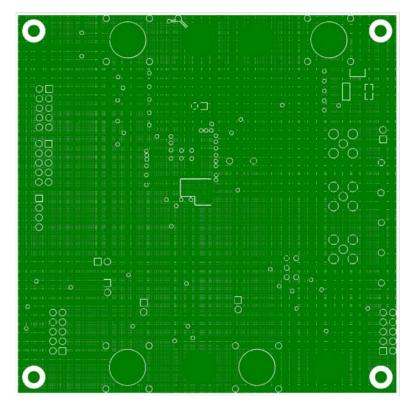


FIGURE 5. INNER\_1

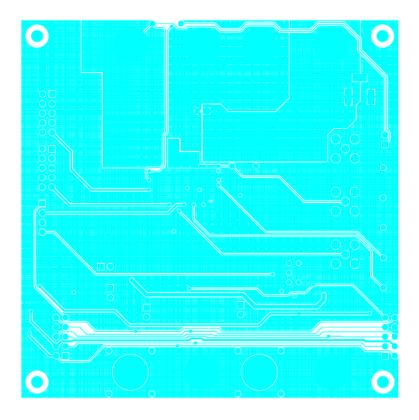


FIGURE 6. INNER\_2

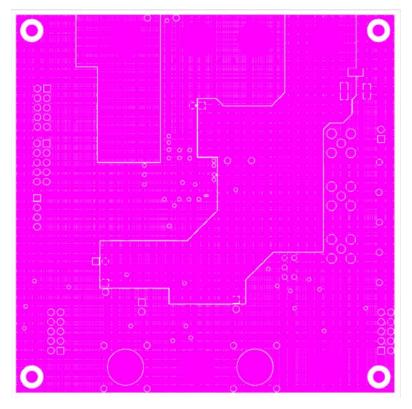


FIGURE 7. INNER\_3

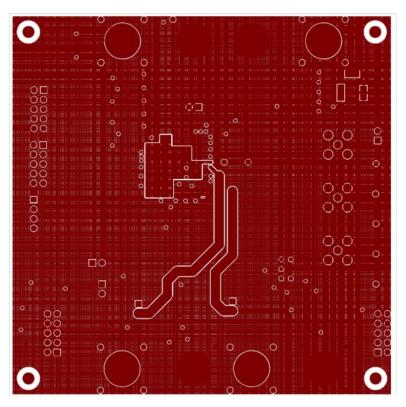


FIGURE 8. INNER\_4

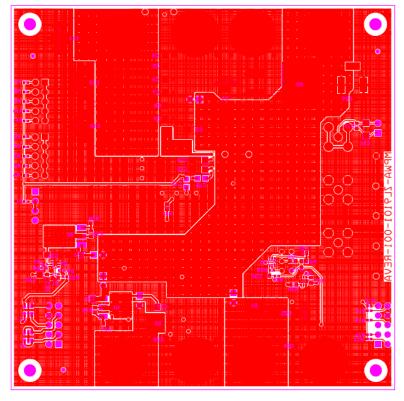


FIGURE 9. BOTTOM

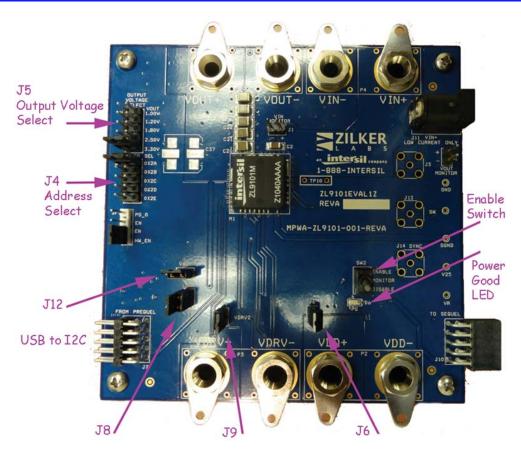


FIGURE 10. PHOTO SHOWING JUMPERS AND CONNECTORS

RENESAS

#### Notice

- 1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system, Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information
- 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application
- 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
- 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
- Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
  - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc. Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or

- 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified
- 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
- e contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
- 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or
- 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
- 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics
- 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



#### SALES OFFICES

## Renesas Electronics Corporation

http://www.renesas.com

Refer to "http://www.renesas.com/" for the latest and detailed information

Renesas Electronics America Inc. 1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A. Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited 9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3 Tel: +1-905-237-2004

Renesas Electronics Europe Limited Dukes Meadow, Milliboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K Tei: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH

Arcadiastrasse 10, 40472 Düsseldorf, German Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China Tel: +86-21-2226-0898, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited

Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong Tel: +852-2265-6688, Fax: +852 2886-9022

Renesas Electronics Taiwan Co., Ltd. 13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan Tel: +886-2-8175-9600, Fax: +886 2-8175-9670

Renesas Electronics Singapore Pte. Ltd.

80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949 Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd. Unit 1207, Block B, Menara Amcorp, Amco Amcorp Trade Centre, No. 18, Jin Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia

Unit 1207, Block B, Menara Amcorp, Amcorp Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd. No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd. 17F, KAMCO Yangiae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea Tel: +82-2-558-3737, Fax: +82-2-558-5338

# **X-ON Electronics**

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Power Management IC Development Tools category:

Click to view products by Renesas manufacturer:

Other Similar products are found below:

EVAL-ADM1168LQEBZ EVB-EP5348UI MIC23451-AAAYFL EV MIC5281YMME EV DA9063-EVAL ADP122-3.3-EVALZ ADP1300.8-EVALZ ADP130-1.2-EVALZ ADP130-1.5-EVALZ ADP130-1.8-EVALZ ADP1714-3.3-EVALZ ADP1716-2.5-EVALZ ADP1740-1.5EVALZ ADP1752-1.5-EVALZ ADP1828LC-EVALZ ADP1870-0.3-EVALZ ADP1871-0.6-EVALZ ADP1873-0.6-EVALZ ADP1874-0.3EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2102-1.25-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2EVALZ ADP2102-3-EVALZ ADP2102-4-EVALZ ADP2106-1.8-EVALZ ADP2147CB-110EVALZ AS3606-DB BQ24010EVM
BQ24075TEVM BQ24155EVM BQ24157EVM-697 BQ24160EVM-742 BQ24296MEVM-655 BQ25010EVM BQ3055EVM

NCV891330PD50GEVB ISLUSBI2CKIT1Z LM2744EVAL LM2854EVAL LM3658SD-AEV/NOPB LM3658SDEV/NOPB LM3691TL1.8EV/NOPB LM4510SDEV/NOPB LM5033SD-EVAL LP38512TS-1.8EV EVAL-ADM1186-1MBZ EVAL-ADM1186-2MBZ