

F&F Filipowski sp. j. Konstantynowska 79/81 95-200 Pabianice phone/fax: (+48 42) 215 23 83 / 227 09 71 POLAND http://www.fif.com.pl e-mail: fif@fif.com.pl

# BISTABLE RELAY

**BIS-408** 


WARRANTY. The F&F products are covered by a warranty of the 24 months from the date of purchase. Effective only with proof of purchase. Contact your dealer of ifferetly with u.s. More information how to make a compliant can be found on the website: <a href="https://www.ffc.com.pl/reklamacie">www.ffc.com.pl/reklamacie</a>





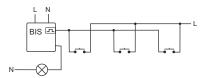
# Purpose

Electronic bistable impulse relay allows switching of lighting or other equipment from several different points of using the control buttons are connected in parallel.



- 1 -

# Wiring diagram

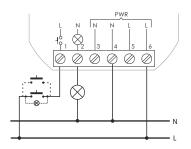

# Power table

-\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\	<b>(</b> )	====		$=$ $\bigcirc$
incandescent	halogen	fluorescent	energy-saving	LED
2000W	1250W	1000W	500W	250W

The above data are indicative and will depend to a large extent on the design of a specific receiver (especially for LED bulbs, energy saving lamps, electronic transformers and pulse power supplies),  $switching \, frequency \, and \, working \, conditions.$ 

- 3 -

For more information visit: www.fif.com.pl.

#### **Functioning**

The receiver is after the current pulse caused by pressing any (bell) connected to the relay. Exclusion the receiver will be the next pulse.

The relay does not have a "memory" of the contact position, ie. in the case of power failure and the subsequent return, contact the relay will be set in the off.

This prevents the automatic switching of loads without supervision after a prolonged power failure.



#### Assembly

- 1. Disconnect the power supply.
- $2. The \, relay \, mounted \, in \, flush-mounted \, box. \,$
- 3. Connect the power supply to a group of PWR: L phase wire to terminal 5 or 6. The N neutral to terminal 3 or 4.
- 4. At the same momentary switches connected to terminal 1 and the L phase conductor.
- 5. Powered receiver connected in series to terminal 2 and the N neutral conductor.

#### Note!

BIS-408 can be used with illuminated buttons.

- 2 -

# Specifications

power supply contact / load current AC-1 current L control pulse response delay	100÷265V AC 1NO / <16A <5mA 0.1÷0.2s
supply signalling	green LED
power consumption	
standby	0.15W
on	0.6W
working temperature	-25÷50°C
terminal	2.5mm <sup>2</sup> screw terminals
tightening torque	0.4Nm
dimensions	Ø54 (□48×43mm), h= 20mm
mounting	in the Ø60 flush-mounted box
ingress protection	IP20

- 4 -

# **X-ON Electronics**

Largest Supplier of Electrical and Electronic Components

Click to view similar products for General Purpose Relays category:

Click to view products by F&F manufacturer:

Other Similar products are found below:

APF30318 JVN1AF-4.5V-F PCN-105D3MHZ 5JO-10000S-SIL 5JO-1000CD-SIL 5JO-400CD-SIL LY2S-AC220/240 LYQ20DC12
6031007G 6131406HQ 6-1393099-3 6-1393099-8 6-1393122-4 6-1393123-2 6-1393767-1 6-1393843-7 6-1415012-1 6-1419102-2 61423698-4 6-1608051-6 6-1608067-0 6-1616170-6 6-1616248-2 6-1616282-3 6-1616348-2 6-1616350-1 6-1616350-8 6-1616358-7 61616359-9 6-1616360-9 6-1616931-6 6-1617039-1 6-1617052-1 6-1617090-2 6-1617090-5 6-1617347-5 6-1617353-3 6-1617801-8 61617802-2 6-1618107-9 6-1618248-4 M83536/1-027M CX-4014 MAHC-5494 MAVCD-5419-6 703XCX-120A 7-1393100-5 7-1393111-7
7-1393144-5 7-1393767-8