

## DEMO CIRCUIT 1197 QUICK START GUIDE

LT3572 Dual Full-Bridge Piezo Driver With 900mA Boost Converter

# DESCRIPTION

Demonstration circuit 1197 features LT3572 in a 800kHz step-up converter circuit, designed for 30V output from a 3V to 5V input. The high output voltage is then used by the dual full-bridge drivers. The LT3572 is capable of independently driving two Piezo motors with two input PWM signals. The motors respond accordingly based on the duty cycle and the frequency of the PWM signals. The drivers operate in an H-bridge fashion, where the OUTA and OUTB pins are the same polarity as the PWMA and PWMB pins respectively and the OUTA and OUTB are inverted from PWMA and PWMB respectively. A PGOOD pin indicates when

the output of the step-up converter is in regulation and the Piezo drivers can start switching. The step-up converter and both Piezo drivers have their own shutdown control.

The LT3572 datasheet gives a complete description of the part, operation and application information. The datasheet must be read in conjunction with this quick start guide for demo circuit 1197.

Design files for this circuit board are available. Call the LTC factory.

 $\checkmark$ , LTC and LT are registered trademarks of Linear Technology Corporation. ThinSOT and PowerPath are trademarks of Linear Technology Corporation.

#### Performance Summary for Piezo Driver ( $T_A = 25^{\circ}C$ )

PARAMETER	CONDITION	VALUE
Minimum Input Voltage		3V
Maximum Input Voltage		5V (Note 1)
Output Voltage V <sub>our</sub>		30V +/-3%
Typical Load		2 TULA50 Piezo Motors
Typical Switching Frequency		800kHz

Note 1: Maximum input voltage of the demo circuit is limited by the voltage rating of the input capacitor.



## QUICK START PROCEDURE

Demonstration circuit 1197 is easy to set up to evaluate the performance of the LT3572. Refer to Figure 1 for proper measurement equipment setup and follow the procedure below:

NOTE. When measuring the input or output voltage ripple, care must be taken to avoid a long ground lead on the oscilloscope probe. Measure the input or output voltage ripple by touching the probe tip directly across the Vin or Vout and GND terminals. See Figure 2 for proper scope probe technique.

- 1. Place JP3, JP4 and JP5 on the ON position:
- 2. Connect the two TULA50 Piezo

Motors to JP1 and JP2.

- 3. With power off, connect the input power supply to Vin and GND.
- 4. Turn on the power at the input.

NOTE. Make sure that the input voltage does not exceed the maximum input voltage.

- 5. Check for the proper output voltage.
- 6. Apply PWM signals, typically switching between 0V and 2V, to the PWMA and PWMB pins.
- 7. Adjust the duty cycles of the input PWM signals and observe the movement of the motors.





Figure 1. Proper Measurement Equipment Setup



Figure 2. Measuring Input or Output Ripple



LT3572





### **X-ON Electronics**

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Power Management IC Development Tools category:

Click to view products by Analog Devices manufacturer:

Other Similar products are found below :

EVAL-ADM1168LQEBZ EVB-EP5348UI MIC23451-AAAYFLEV MIC5281YMMEEV DA9063-EVAL ADP122-3.3-EVALZ ADP130-0.8-EVALZ ADP130-1.2-EVALZ ADP130-1.5-EVALZ ADP130-1.8-EVALZ ADP1714-3.3-EVALZ ADP1716-2.5-EVALZ ADP1740-1.5-EVALZ ADP1752-1.5-EVALZ ADP1828LC-EVALZ ADP1870-0.3-EVALZ ADP1871-0.6-EVALZ ADP1873-0.6-EVALZ ADP1874-0.3-EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2102-1.25-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2102-1.25-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP2102-3-EVALZ ADP2102-4-EVALZ ADP2106-1.8-EVALZ ADP2147CB-110EVALZ AS3606-DB BQ24010EVM BQ24075TEVM BQ24155EVM BQ24157EVM-697 BQ24160EVM-742 BQ24296MEVM-655 BQ25010EVM BQ3055EVM NCV891330PD50GEVB ISLUSBI2CKIT1Z LM2744EVAL LM2854EVAL LM3658SD-AEV/NOPB LM3658SDEV/NOPB LM3691TL-1.8EV/NOPB LM4510SDEV/NOPB LM5033SD-EVAL LP38512TS-1.8EV EVAL-ADM1186-1MBZ EVAL-ADM1186-2MBZ