QUICK START GUIDE FOR DEMONSTRATION CIRCUIT 660 LOW NOISE MICROPOWER LINEAR VOLTAGE REGULATOR

LTC1844

DESCRIPTION

Demonstration circuit DC660 is a low noise micropower voltage regulator using the LTC1844 ultra-low dropout CMOS linear regulator, which comes in a tiny 5-Pin SOT-23 package. The DC660 has an input voltage range from 1.8V to 6.5V, and is capable of delivering 150 mA max. The DC660 is able to use ceramic capacitors, due to the LTC1844 capability of maintaining stability with ultra-low ESR capacitors. With the

QUICK START PROCEDURE

DC660 is easy to set up for evaluating the performance of the LTC1844. For proper measurement equipment configuration, set up the circuit according to the diagram in **Figure 1**.

Please follow the procedure outlined below for proper operation.

- 1. Before proceeding to test, insert jumper JP1 into the 1.5V option and apply no load across Vout.
- 2. Apply 1.6V across Vin (to Gnd). Draw 10mA of load current. Measure Vout; it should be 1.5V +/- 2% (1.47V to 1.53V).
- 3. Vary the input voltage from 1.6V to 6.5V and the load current from 10 mA to 100 mA. Vout should measure 1.5V +/- 4% (1.44V to 1.56V).
- 4. Turn off the input power and move jumper JP1 into any of the remaining output voltage options: 1.8V, 2.5V, 2.8V, or 3.3V. Re-apply

small size ceramic capacitors, tiny SOT-23 package of the LTC1844, plus its low quiescent current – maximum 80uA over temperature, the DC660 voltage regulator is ideally suited for hand-held applications, such as cellular phones or PDAs.

Gerber files for this circuit are available. Call the LTC Factory.

power, and, just as in the 1.5V test, the output voltage should read Vout +/- 2% tolerance under static line and load conditions, and +/- 4% tolerance under dynamic line and load conditions.

5. When finished evaluating, turn off the input power.

Warning - If long leads are used to power the demo circuit, the input voltage at the part could "ring". This ringing could affect the operation of the circuit or even exceed the maximum voltage rating of the IC. To eliminate this, insert a small tantalum capacitor (for instance. an AVX part TAJW226M010R) on the pads between the input power and return terminals on the bottom of the demo board. The (greater) ESR of the tantalum will dampen the (possible) ringing voltage due to the use of long input leads. On a normal, typical PCB, with short traces, the capacitor is not needed.

QUICK START GUIDE FOR DEMONSTRATION CIRCUIT 660 LOW NOISE MICROPOWER LINEAR VOLTAGE REGULATOR

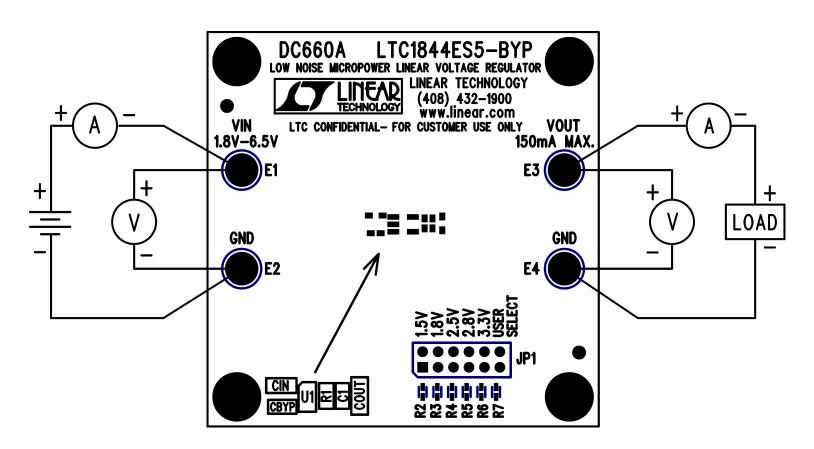


Figure 1. Proper Measurement Equipment Setup


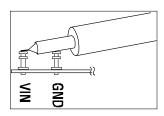


Figure 2. Measuring Input or Output Ripple

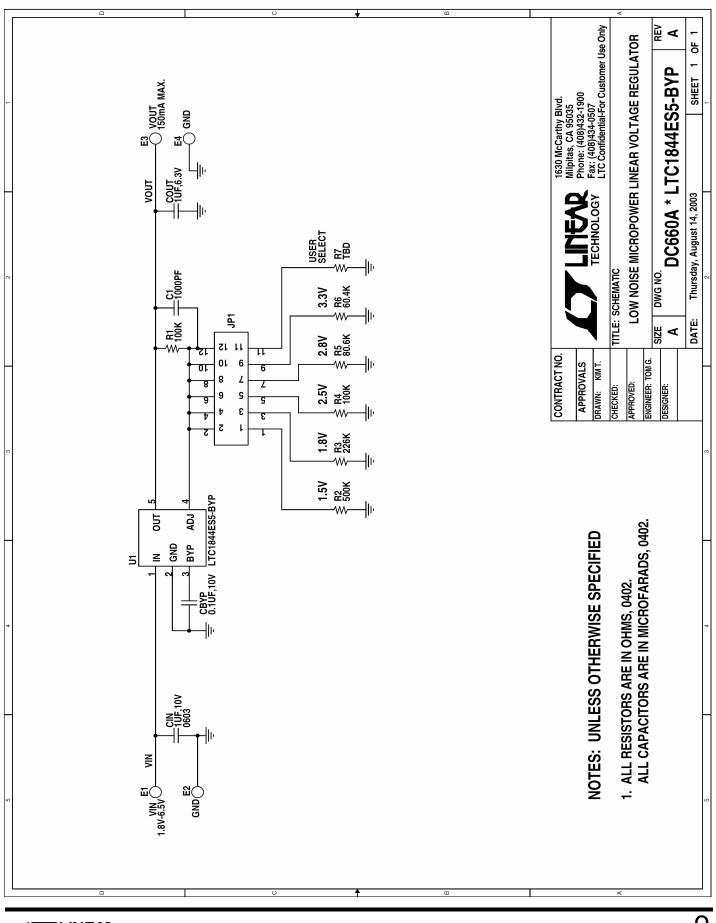QUICK START GUIDE FOR DEMONSTRATION CIRCUIT 660 LOW NOISE MICROPOWER LINEAR VOLTAGE REGULATOR



LINEAR TECHNOLOGY 3

X-ON Electronics

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Power Management IC Development Tools category:

Click to view products by Analog Devices manufacturer:

Other Similar products are found below :

EVAL-ADM1168LQEBZ EVB-EP5348UI MIC23451-AAAYFLEV MIC5281YMMEEV DA9063-EVAL ADP122-3.3-EVALZ ADP130-0.8-EVALZ ADP130-1.2-EVALZ ADP130-1.5-EVALZ ADP130-1.8-EVALZ ADP1714-3.3-EVALZ ADP1716-2.5-EVALZ ADP1740-1.5-EVALZ ADP1752-1.5-EVALZ ADP1828LC-EVALZ ADP1870-0.3-EVALZ ADP1871-0.6-EVALZ ADP1873-0.6-EVALZ ADP1874-0.3-EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2102-1.25-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2106-1.8-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP2102-3-EVALZ ADP2102-4-EVALZ ADP2106-1.8-EVALZ ADP2147CB-110EVALZ AS3606-DB BQ24010EVM BQ24075TEVM BQ24155EVM BQ24157EVM-697 BQ24160EVM-742 BQ24296MEVM-655 BQ25010EVM BQ3055EVM NCV891330PD50GEVB ISLUSBI2CKIT1Z LM2744EVAL LM2854EVAL LM3658SD-AEV/NOPB LM3658SDEV/NOPB LM3691TL-1.8EV/NOPB LM4510SDEV/NOPB LM5033SD-EVAL LP38512TS-1.8EV EVAL-ADM1186-1MBZ EVAL-ADM1186-2MBZ