QUICK START GUIDE FOR DEMONSTRATION CIRCUIT 704 DUAL OUTPUT LOW NOISE LDO REGULATORS

LT3023

DESCRIPTION

Demonstration circuit 704 is a dual output regulator based on the LT3023 IC, which consists of two identical LDO linear regulators. The DC704 has an input voltage range of 2.3V to 20V, and either output is capable of delivering up to 100mA of output current. The DC supply current is typically only 20uA (per channel) at no load. The LT3023 comes in a small 10-pin DFN package, which has an exposed pad on the bottom-side of the IC for better thermal performance. DC704 comes installed with ceramic capaci-

QUICK START PROCEDURE

DC704 is easy to set up to evaluate the performance of the LT3023. Refer to Figure 1 for proper measurement equipment setup and follow the procedure outlined below for proper operation.

- 1. Connect the input power supply to the VIN and GND terminals. Connect the loads between the VOUT and GND terminals.
- 2. Before proceeding to operation, insert jumpers JP3 and JP4 into the OFF positions, jumpers JP1 and JP2 into the voltage options of choice (2.5V, 3.3V, and 5V).
- 3. Apply 6.5V at VIN. Measure both VOUT1 and VOUT2; they should read 0V.
- 4. Turn on VOUT1 and VOUT2 by moving jumpers JP3 and JP4 from the OFF position to the ON position. Both output voltages should be within a tolerance of +/- 2%.
- 5. Vary the input voltage from 6.5V to 20V. Both output voltages should be within +/- 3.3% tolerance.

tors, because of the LT3023 ability of maintaining stability with ceramic output capacitors. There are ceramic bypass capacitors on each output for extra low noise performance. These features make the DC704 an ideal circuit for use in battery-powered, hand-held applications or noise sensitive applications.

Design files for this circuit are available. Call the LTC Factory.

- 6. Vary each load current from 0 to 100mA. Both output voltages should be within a toler-ance of $\pm -4\%$.
- 7. Observe both output voltages AC-coupled; they should measure noise voltages of less than 2mVAC each. Refer to Figure 2 for proper measurement technique.
- 8. When finished, move jumpers JP3 and JP4 to the OFF position and disconnect the power.

Warning - if long leads are used to power the demo circuit, the input voltage at the part could "ring", which could affect the operation of the circuit or even exceed the maximum voltage rating of the IC. To eliminate the ringing, insert a small tantalum capacitor (for instance, an AVX part # TAJW106M025R) on the pads between the input power and return terminals on the bottom of the demo board. The (greater) ESR of the tantalum will dampen the (possible) ringing voltage due to the use of long input leads. On a normal, typical PCB, with short traces, the capacitor is not needed.

QUICK START GUIDE FOR DEMONSTRATION CIRCUIT 704 DUAL OUTPUT LOW NOISE LDO REGULATORS

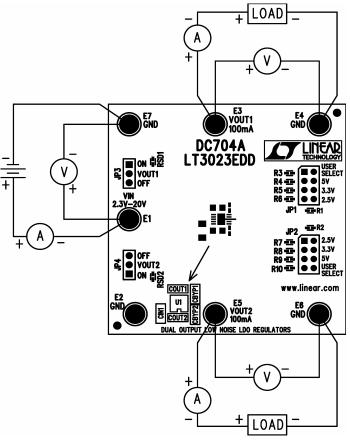


Figure1. Proper Measurement Equipment Setup


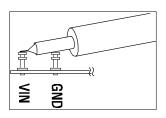


Figure 2. Measuring Input or Output Ripple

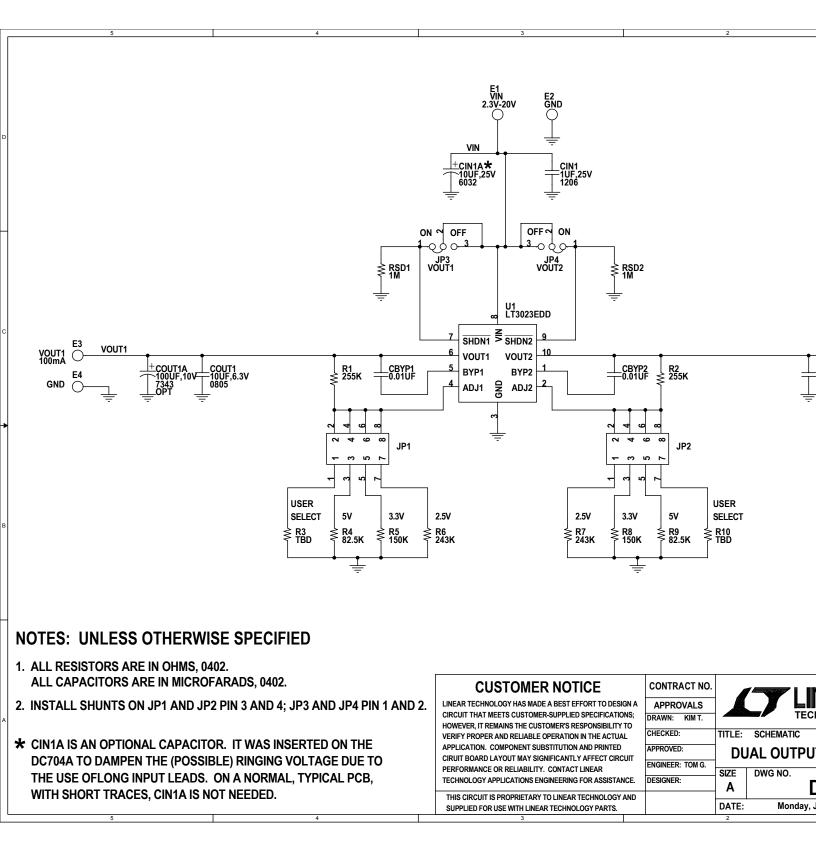



Linear Technology Corporation LT3023EDD

DUAL OUTPUT LOW NOISE LDO REGULATORS ENG: TOM GROSS (23-30)

ltem	Qty	Reference	Part Description	Manufacture / Par
1	2	CBYP2,CBYP1	CAP., X7R, 0.01UF 16V, 20%, 0402	AVX, 0402YC103MAT
2	1	CIN1	CAP., X7R, 1UF 25V, 20%, 1206	AVX, 12063C105MAT
3	1	CIN1A	CAP., TANT 10UF 25V, 20%, 6032	AVX, TAJW106M025R
4	0	COUT1A,COUT2A	CAP., TANT 100UF 10V, 7343	AVX, TPSD107M010R0100 OF
5	2	COUT2,COUT1	CAP., X5R, 10UF 6.3V, 20%, 0805	TAIYO YUDEN, JMK212BJ106M
6	7	E1-E7	TESTPOINT, TURRET, .094"	MILL-MAX, 2501-2
7	2	JP1,JP2	JMP, 2X4, .079CC, HD2X4-079	COMM-CON, 2202S-08-G2
8	2	JP3,JP4	HEADER, 3PIN 1 ROW .079CC	COMM-CON, 2802S-03-G1
9	4	SHUNTS FOR JP1-JP4	SHUNT, .079" CENTER	COMM-CON CCIJ2MM-138G
10	2	RSD2,RSD1	RES., CHIP 1M 1/16W 5%,0402	AAC, CR05-105JM
11	2	R1,R2	RES., CHIP 255K 1/16W 1%,0402	AAC, CR05-2553FM
12	0	R10,R3	RES., CHIP, 0402	TBD
13	2	R9,R4	RES., CHIP 82.5K 1/16W 1%,0402	AAC, CR05-8252FM
14	2	R5,R8	RES., CHIP 150K 1/16W 1%,0402	AAC, CR05-1503FM
15	2	R7,R6	RES., CHIP 243K 1/16W 1%,0402	AAC, CR05-2433FM
16	1	U1	I.C., LT3023EDD, DFN10DD	LINEAR TECH., LT3023EDD

X-ON Electronics

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Power Management IC Development Tools category:

Click to view products by Analog Devices manufacturer:

Other Similar products are found below :

EVAL-ADM1168LQEBZ EVB-EP5348UI MIC23451-AAAYFLEV MIC5281YMMEEV DA9063-EVAL ADP122-3.3-EVALZ ADP130-0.8-EVALZ ADP130-1.2-EVALZ ADP130-1.5-EVALZ ADP130-1.8-EVALZ ADP1714-3.3-EVALZ ADP1716-2.5-EVALZ ADP1740-1.5-EVALZ ADP1752-1.5-EVALZ ADP1828LC-EVALZ ADP1870-0.3-EVALZ ADP1871-0.6-EVALZ ADP1873-0.6-EVALZ ADP1874-0.3-EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2102-1.25-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2106-1.8-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP2102-3-EVALZ ADP2102-4-EVALZ ADP2106-1.8-EVALZ ADP2147CB-110EVALZ AS3606-DB BQ24010EVM BQ24075TEVM BQ24155EVM BQ24157EVM-697 BQ24160EVM-742 BQ24296MEVM-655 BQ25010EVM BQ3055EVM NCV891330PD50GEVB ISLUSBI2CKIT1Z LM2744EVAL LM2854EVAL LM3658SD-AEV/NOPB LM3658SDEV/NOPB LM3691TL-1.8EV/NOPB LM4510SDEV/NOPB LM5033SD-EVAL LP38512TS-1.8EV EVAL-ADM1186-1MBZ EVAL-ADM1186-2MBZ