

LT3482

DC/DC Boost Converter for APD Bias

DESCRIPTION

Demonstration circuit 975A is a DC/DC Converter for APD Bias featuring the LT3482 in a 3mm x 3mm QFN package. This demo circuit is designed to convert a 3V-12V source to 80V at 2mA. The circuit runs at 1.1MHz but can be easily programmed to run at 650KHz (inductor and other components might need to change for such case). The LT3482 features a 48V, 260mA switch, integrated Schottky diodes and a high side current monitor which provides a current proportional to the APD current. This current can be used as a reference to digitally program the output via the CTRL pin. This circuit is specifically designed for APD bias and is optimized for performance, solution size and profile. To further reduce the solution size, inductors such as Taiyo Yuden BRL2012B type can be used though efficiency will suffer about 10%. Typical applications include APD bias, PIN Diode Bias, Optical Receivers and Modules, Fiber Optic Network Equipment etc.

Design files for this circuit board are available. Call the LTC factory.

LT is a registered trademark of Linear Technology Corporation.

PERFORMANCE SUMMARY DC975A Specifications are at TA = 25℃

SYMBOL	PARAMETER	CONDITIONS	MIN	TYP	MAX	UNITS
V _{IN}	Input Supply Range		3		12	V
V _{OUT}	Output Voltage Range	V _{IN} = 3V, I _{LOAD} = 2mA	75	80	85	V
V _{OUT}	Output Voltage Range	$V_{IN} = 12V, I_{LOAD} = 2mA$	75	80	85	V
RIPPLE		$V_{IN} = 3.6V, I_{LOAD} = 2mA$		500		μV
FS	Switching frequency			1.1		MHz

QUICK START PROCEDURE

Demonstration circuit 975 is easy to set up to evaluate the performance of the LT3482. Refer to Figure 1. for proper measurement equipment setup and follow the procedure below:

NOTE. When measuring the output voltage ripple, use a BNC cable to connect J1 to the oscilloscope. Set the oscilloscope to AC couple, 2mV/division. That should yield the results shown in Figure 2 (Make sure there are no test cables connected to the APD node).

1. Place jumper in the following position:

JP1 Run

2. With power off, connect the input power supply to Vin and GND.

- **3.** Connect a 40K resistor from APD to GND.
- 4. Turn on the power at the input.
- **5.** Check for the proper output voltage. Vout1 = 75V to 85V.

NOTE. If there is no output, temporarily disconnect the load to make sure that the load is not set too high.

6. Once the proper output voltage is established, adjust the load within the operating range and observe the output voltage regulation, ripple voltage, efficiency and other parameters.



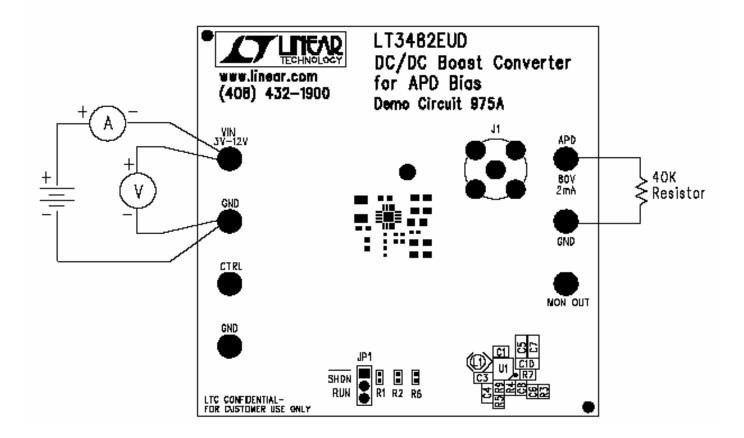


Figure 1. Proper Measurement Equipment Setup




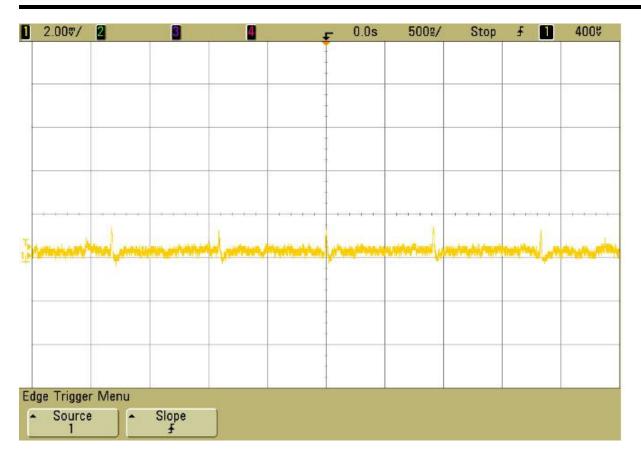


Figure 2. Output Ripple measured with BNC cable directly connected to oscilloscope. BW=20MHz. 2mV/div

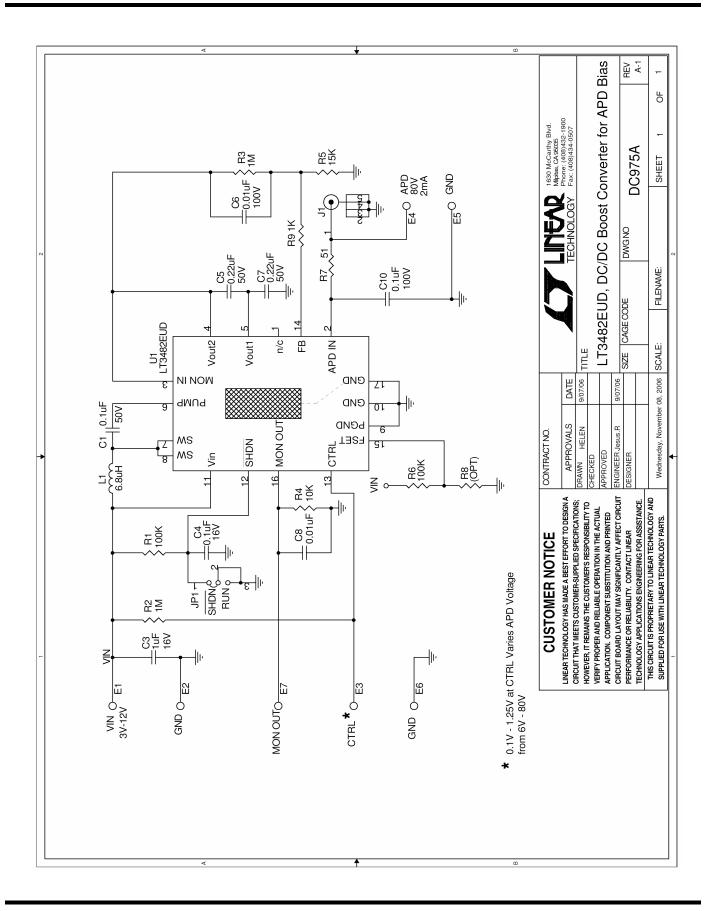

LT3482





4

TECHNOLOGY

Bill Of Material Demo Bd. #975A 1/19/2007

			International / Fart #
	REQUIRED CIRCUIT COMPONENTS:	VENTS:	
- -	CI	CAP., X7R, 0.1uF, 50V,10%, 0603	TDK, C1608X7R1H104K
2	C3	CAP., X7R, 1uF, 16V, 20%, 0603	TDK, C1608X7R1C105M
ი ო	C4	CAP., X7R, 0.1uF, 16V, 10%, 0603	AVX, 0603YC104KAT2A
4	C5,C7	CAP., X7R, 0.22uF, 50V,10%, 0805	TAIYO YUDEN, UMK212BJ224MG
1	C6	CAP., X7R, 0.01uF, 100V, 10%, 0805	AVX, 08051C103KAT
9	C8	CAP., X7R, 0.01uF, 16V, 20%, 0402	AVX., 0402YC103MAT2A
7	C10	CAP., X7R, 0.1uF, 100V, 20%, 0805	TDK, C2012X7R2A104M
8	L1	INDUCTOR., 6.8uH	COILTRONICS, SD3110-6R8-R
9	R1,R6	RES., CHIP, 100K, 1/16W, 5% , 0402	VISHAY, CRCW0402104JRT6
10	R2	RES., CHIP, 1M, 1/16W, 1% , 0402	VISHAY, CRCW04021004FRT6
1	R3	RES., CHIP, 1M, 1/10W, 1% , 0805	VISHAY, CRCW08051004FRT6
12 1	R4	RES., CHIP, 10K, 1/16W, 1% , 0402	VISHAY, CRCW040210K0FKED
13 1	R5	RES., CHIP, 15.8K, 1/16W, 1% , 0402	VISHAY, CRCW040215K8FKED
14 1	R7	RES., CHIP, 51, 1/16W, 5% , 0402	VISHAY, CRCW040251R0JNED
15 1	R9	RES., CHIP, 1K, 1/16W, 5% , 0402	VISHAY, CRCW04021K00JNED
16 1	U1	I.C., LT3482EUD#PBF,3X3mm,QFN	LINEAR TECH, LT3482EUD#PBF
	ADDITIONAL DEMO BOARD	MO BOARD CIRCUIT COMPONENTS:	
-	R8(OPT)	RES., 0402	
	HARDWARE-FOR DEMO BO/	DEMO BOARD ONLY:	
1 7	E1-E7	TESTPOINT, TURRET, .095"	MILL-MAX, 2501-2-00-80-00-70-0
2 1	J1	CONN, BNC, 5PINS	CONNEX, 112404
3 1	JP1	0.079 SINGLE ROW HEADER, 3 PIN	SAMTEC, TMM-103-02-L-S
4 1	JP1	SHUNT	SAMTEC, 2SN-BK-G



X-ON Electronics

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Power Management IC Development Tools category:

Click to view products by Analog Devices manufacturer:

Other Similar products are found below :

EVAL-ADM1168LQEBZ EVB-EP5348UI MIC23451-AAAYFLEV MIC5281YMMEEV DA9063-EVAL ADP122-3.3-EVALZ ADP130-0.8-EVALZ ADP130-1.2-EVALZ ADP130-1.5-EVALZ ADP130-1.8-EVALZ ADP1714-3.3-EVALZ ADP1716-2.5-EVALZ ADP1740-1.5-EVALZ ADP1752-1.5-EVALZ ADP1828LC-EVALZ ADP1870-0.3-EVALZ ADP1871-0.6-EVALZ ADP1873-0.6-EVALZ ADP1874-0.3-EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2102-1.25-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP1882-1.0-EVALZ ADP199CB-EVALZ ADP2106-1.8-EVALZ ADP2102-1.875EVALZ ADP2102-1.8-EVALZ ADP2102-2-EVALZ ADP2102-3-EVALZ ADP2102-4-EVALZ ADP2106-1.8-EVALZ ADP2147CB-110EVALZ AS3606-DB BQ24010EVM BQ24075TEVM BQ24155EVM BQ24157EVM-697 BQ24160EVM-742 BQ24296MEVM-655 BQ25010EVM BQ3055EVM NCV891330PD50GEVB ISLUSBI2CKIT1Z LM2744EVAL LM2854EVAL LM3658SD-AEV/NOPB LM3658SDEV/NOPB LM3691TL-1.8EV/NOPB LM4510SDEV/NOPB LM5033SD-EVAL LP38512TS-1.8EV EVAL-ADM1186-1MBZ EVAL-ADM1186-2MBZ