

Features

RoHS compliant*

- Low capacitance <5 pF</p>
- ESD protection
- Surge protection


This series is currently available, but is not recommended for new designs. The Model TISP4G024L1 is the recommended pin-to-pin replacement.

CDSOT236-DSL03xx - TVS Diode Array Series

General Information

The CDSOT236-DSL03xx device provides ESD, EFT and surge protection for highspeed data ports to assist in meeting IEC 61000-4-2 (ESD), IEC 61000-4-4 (EFT) and IEC 61000-4-5 (Surge) requirements. The Transient Voltage Suppressor array is available with a Working Peak Reverse Voltage of 12 V or 24 V.

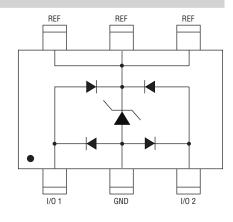The SOT23-6L packaged device will mount directly onto the industry standard SOT23-6L footprint and is easy to handle with standard pick and place equipment.



Absolute Maximum Ratings, T_A = 25 °C (Unless Otherwise Noted)

Detin a	Cumhal	CDSC	L I with		
Rating	Symbol	DSL0312 DSL0324		Unit	
Working Peak Voltage	VWM	12	24	V	
Peak Pulse Current (t _p = 8/20 μs)	IPPM	35	15	A	
Peak Pulse Power ($t_p = 8/20 \ \mu s$)	PPP	500		W	
ESD (IEC61000-4-2 Contact)		٤	kV		
ESD (IEC61000-4-2 Air)		1	kV		
Operating Temperature	Т	-40 to	°C		
Storage Temperature	T _{STG}	-55 to	°C		

Electrical Characteristics, T_A = 25 °C (Unless Otherwise Noted)

Para	neter	Test Condition (Note 1)		Min.	Тур.	Max.	Unit
V _{BR} Breakdown Voltage	I _{BR} = 1 mA	'DSL0312	14			V	
		'DSL0324	26				
V _C Clamping Voltage	Ι _P = 1 A, 8/20 μs	'DSL0312		18	20	v	
		'DSL0324		31	38		
V _C Clamping Voltage	I _P = 10 A, t _w = 1 μs	'DSL0312		21		v	
		'DSL0324		37			
V _C Clamping Voltage	I _P = 35 A, 8/20 μs	'DSL0312		34		V	
	I _P = 15 A, 8/20 μs	'DSL0324		40			
ID Leakage C	urrent	$V_D = V_{WM}$				100	nA
C Capacitance	е	V _D = 1 V, f = 10 MHz, 1 Vrms			1.4	5	pF
∆C Capacitanc	e Variation	$V_D = 1 V$ to V_{WM} , f = 10 MHz, 1 Vrms			0.2	2	pF

Note 1: All measurements made between I/O 1 and I/O 2.

*RoHS Directive 2002/95/EC Jan. 27, 2003 including annex and RoHS Recast 2011/65/EU June 8, 2011. Specifications are subject to change without notice.

The device characteristics and parameters in this data sheet can and do vary in different applications and actual device performance may vary over time. Users should verify actual device performance in their specific applications.

Applications


- ADSL / VDSL cards
- Personal Digital Assistants (PDAs)
- Mobile phones and accessories
- Portable electronics

CDSOT236-DSL03xx - TVS Diode Array Series


BOURNS

Performance Graphs


Maximum Current vs. Pulse Duration

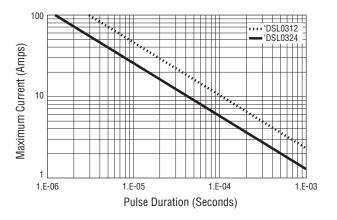

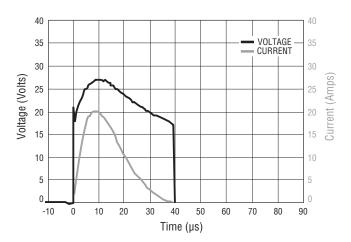
Clamping Waveform for 'DSL0312 During a 20 A, 8/20 µs Surge



Normalized Capacitance vs. V_D

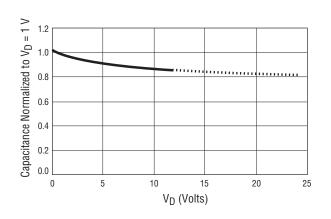

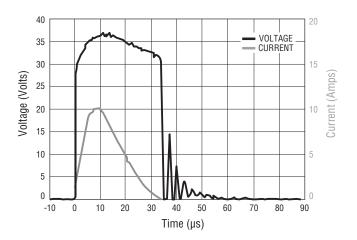Clamping Waveform for 'DSL0324 During a 10 A, 8/20 µs Surge



Bourns

Application Information

Communication systems with exposed signal lines are often subjected to high level transient threats. The CDSOT236-DSL03xx family of devices was designed to help protect signal lines from threats such as those defined in Telcordia GR-1089 and ITU-T.

Figure 1 shows the CDSOT236-DSL03xx TVS diode array used in a design topology that protects a VDSL driver. The diode array limits the peak differential voltage across the VDSL driver outputs. The current limiting resistors (R_p), typically about 1 ohm, limit the peak current seen by the driver. Low voltage varistors MOV1 and MOV2, with a typical working voltage of less than 20 V, limit the current in the line side of the transformer by limiting the voltage across it. Exact values for the current limiting resistors and the varistors are dependent on the characteristics of the transformer as well as the sensitivity of the driver to overvoltage/ overcurrent conditions. The use of primary protectors downstream from the device will also influence the requirements for this protection circuit design. In applications sensitive to very low levels of leakage current, optional bias resistors R_{B1} and R_{B2} can be used. Both resistors would be required for dual supply applications. Only R_{B1} is required for single supply applications. In this case, the anodes of the diode array should be connected to ground.

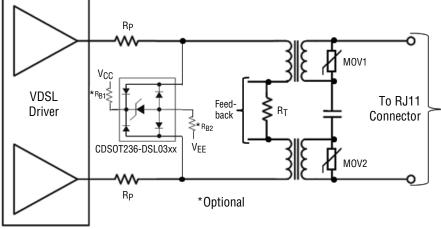


Figure 1. VDSL Driver Protection Design Topology

When routing differential signal traces on the PCB, such as in a VDSL application, it is important to maintain symmetry in the routing. Figure 2 below shows an example of how differential traces that connect to the CDSOT236-DSL03xx TVS diode array can be routed. As the signal traces approach the diode array

the traces should be flared out to make the connections with the device and then brought back together on the opposite side of the device. Routing to the next destination would continue from there.

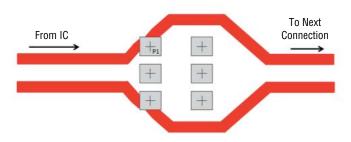


Figure 2. Connecting a Differential Signal to the Model CDSOT236-DSL03xx

Specifications are subject to change without notice. The device characteristics and parameters in this data sheet can and do vary in different applications and actual device performance may vary over time. Users should verify actual device performance in their specific applications.

Bourns

Application Information (Continued)

In applications where the current limiting resistors (R_P in Figure 1) cannot reduce the current into (or out of) the driver to an acceptable level, the resistors can be replaced with a Bourns[®] Transient Current Suppressor (TCS[™]) device as shown in Figure 3. The Model TCS-DL004-750-WH shown in Figure 3 is a dual channel device that has a nominal series resistance of only 1 ohm. The resistance between the two channels is very well matched with a nominal maximum difference of + 0.02 ohms

between the channels. This device has a nominal trigger current of 1.1 amps. The current through the device would be limited to this level with up to 40 V across this device, making it dramatically more effective than a 1 ohm series resistor. Devices with different trigger levels and series resistances are also available. For additional information on the TCS™ family of devices, please consult the data sheets on our website at http://www.bourns.com/ ProductLine.aspx?name=transient_current_suppressors.

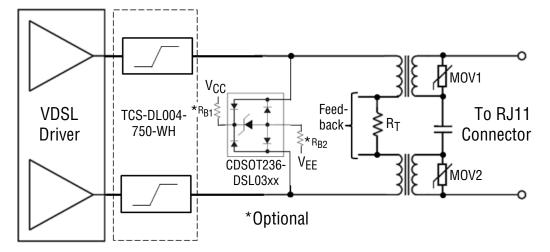


Figure 3. VDSL Driver Protection Design with Transient Current Suppressor Technology

Figure 4 shows how the trace routing should be done when the TCS[™] device is used in conjunction with the CDSOT236-DSL03xx TVS diode array.


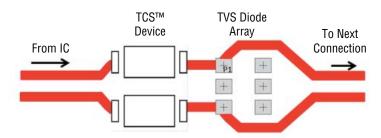



Figure 4. Connecting a Differential Signal to the Model CDSOT236-DSL03xx and TCS™ Device

BOURNS


Product Dimensions

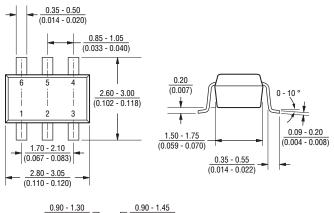This is a molded SOT23-6L package with RoHS compliant 100 % Matte Sn on the lead frame. It weighs approximately 15 mg and has a flammability rating of UL 94V-0.



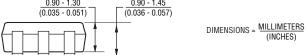

Recommended Footprint

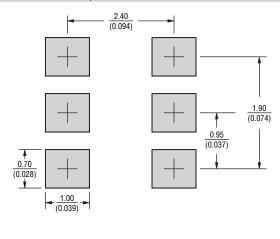

DIMENSIONS = MILLIMETERS (INCHES)


Typical Part Marking

CDSOT236-DSL0312L	2
CDSOT236-DSL0324L	4

How to Order

1


(INCHES)

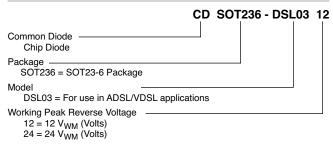


Bourns

Packaging Information

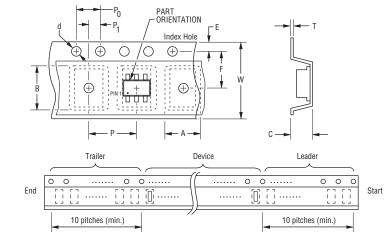The product is packaged in tape and reel format per EIA-481 standard.



Direction of Feed

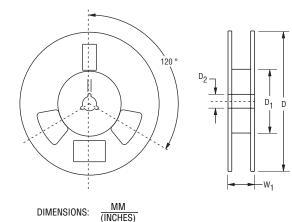

Item Symbol SOT23-6 3.90 ± 0.10 Carrier Width А (0.154 ± 0.004) 3.90 ± 0.10 Carrier Length В (0.154 ± 0.004) 0.90 ± 0.10 Carrier Depth С $\overline{(0.035 \pm 0.004)}$ 1.55 ± 0.05 Sprocket Hole d (0.061 ± 0.002) 178 Reel Outside Diameter D (7.008) 50.0 $\frac{30.0}{(1.969)}$ MIN. **Reel Inner Diameter** D₁ 13.0 ± 0.20 Feed Hole Diameter D_2 (0.512 ± 0.008) 1.75 ± 0.10 Sprocket Hole Position Е (0.069 ± 0.004) 3.50 ± 0.05 Punch Hole Position F (0.138 ± 0.002) 4.00 ± 0.10 Punch Hole Pitch Ρ (0.157 ± 0.004) 4.00 ± 0.10 Sprocket Hole Pitch P₀ (0.157 ± 0.004) 2.00 ± 0.05 **Embossment Center** P₁ (0.079 ± 0.002) $\frac{0.20 \pm 0.10}{(0.008 \pm 0.004)}$ **Overall Tape Thickness** Т 8.00 ± 0.20 Tape Width W (0.315 ± 0.008) 14.4 Reel Width W₁ MAX. (0.567)Quantity per Reel 3000 ---

BOURNS®

Asia-Pacific: Tel: +886-2 2562-4117 • Fax: +886-2 2562-4116 EMEA: Tel: +36 88 520 390 • Fax: +36 88 520 211 The Americas: Tel: +1-951 781-5500 • Fax: +1-951 781-5700 www.bourns.com

REV. 11/15

Specifications are subject to change without notice.

The device characteristics and parameters in this data sheet can and do vary in different applications and actual device performance may vary over time. Users should verify actual device performance in their specific applications.

X-ON Electronics

Largest Supplier of Electrical and Electronic Components

Click to view similar products for TVS Diode Arrays category:

Click to view products by Bourns manufacturer:

Other Similar products are found below :

D1213A-04SO-7 D5V0F4U5P5-7 SZMMQA6V2TIG 409031D USB50805e3/TR7 D3V3Q1B2DLP3-7 D55V0M1B2WS-7 DRTR5V0U4SL-7 SZMMQA33VT1G IP4042CX5/LF,135 D1213A-01LP4-7B D1213A-02WL-7 MAX3203EEWT+T D5V0F4U10MR-13 RSA6.1J4T2R NUP4103FCT1G NUP5150MUTBG SZMMBZ12VALT1G 82401646 PESD1CANVL D1213A-01W-7 PESD1FLEX,215 ESDR0544MDMR4G ESDR0502BT1G ESD7M5.0DT5G ESD5V5U5ULCE6327HTSA1 ESD1P0RFWH6327XTSA1 SMF05CT2G MAX3203EETTT NUP4102XV6T1G D5V0L4B5TS-7 NUP4060AXV6T1G SZMMBZ15VDLT1G SZMMBZ15VALT1G SRDA3.3-4BTG SPT01-335DEE SMS24CT1G SMF15CT1G MG2040MUTAG PLCDA15C6LF NUP5120X6T2G PACDN1408CG ESDA5V3SC6Y SNUP2114UCMR6T1G SZNSQA6V8AW5T2G SZSMF12CT1G SP6001-06UTG-1 031-2 CDSOT23-SRV05-4 ESD7C33DT5G