Serial 7-Seg Display[™]

Manual

All Mikroelektronika's development systems feature a large number of peripheral modules expanding microcontroller's range of application and making the process of program testing easier. In addition to these modules, it is also possible to use numerous additional modules linked to the development system through the I/O port connectors. Some of these additional modules can operate as stand-alone devices without being connected to the microcontroller.

Additional Board

Serial 7-Seg Display Additional Board

The Serial 7-Seg Display additional board is used to display digits on seven-segment displays. Communication between the additional board and a microcontroller is performed via a Serial Peripheral Interface (SPI), whereas four 7-segment displays on the additional board are used to display digits.

How to connect the board?

The additional board is connected to a development system via an IDC10 connector on the board and a 2x5 connector on one of the developmet system's ports. It is necessary to define in the program, to be loaded into the microcontroller, which port will be used for SPI communication.

The position of SMD jumpers depends on the development system in use, Figure 3. These jumpers are placed in the position marked PIC by default. It means that the board is ready to be used with PIC development systems. If you want to use it with AVR/8051 development systems, it is necessary to unsolder jumpers from the PIC position and resolder them in the AVR/8051 position.

The Serial 7-Seg Display additional board is powered with the 5V power supply from the development system it is connected to.



Figure 1: Serial 7-Seg Display additional board

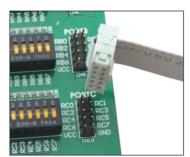


Figure 2: Connecting IDC10 connector

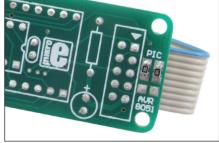


Figure 3: Development system selection

How does the board operate?

In order to use this additional board, it is necessary to load a .hex code into the microcontroller on the devlopment system. Find examples of .hex code that may be loaded into the microcontroller on our web site:

http://www.mikroe.com/eng/products/view/162/serial-7-seg-display-board/

As a result of the .hex code loading, the development system starts communication with the additional board via a Serial Peripheral Interface (SPI).

Displaying digits is enabled by the time-division multiplexing. All the operations related to multiplexing and displaying digits are performed by using the MAX7219 circuit provided on the additional board. The time-division multiplexing of a 7-segment display is based on fast turning the display segments on/off in such a manner that one gets impression that all eight digits are active at the same time. The MAX7219 circuit feeds digit segments with a signal via pins marked SEGxx, whereas pins marked DIGx are used to select one of four displays to show the appropriate number.

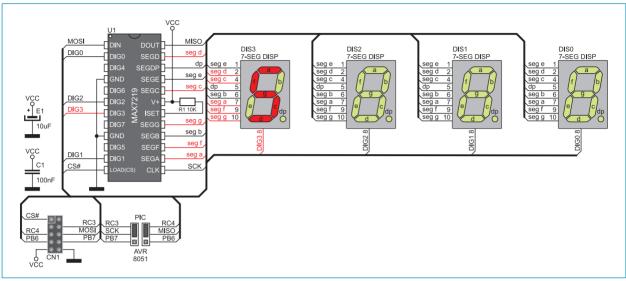


Figure 4: Time-division multiplexing performed on the DIS3 display

In Figure 4, signals provided by the MAX7219 circuit causes segments of the DIS3 display to show number 5. When this display turns off, the MAX7219 circuit sends a signal to the next display (DIS2), via the DIG2 pin, to show number 6. The same applies to digits DIS1 and DIS0. When one cycle is complete, another one automatically starts, which results in successive changing of display digits DIS3, DIS2, DIS1 and DIS0.

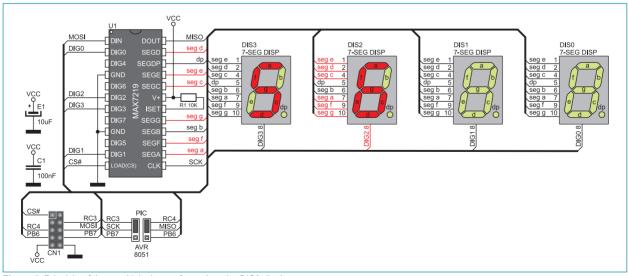


Figure 5: Principle of time-multiplexing performed on the DIS2 display

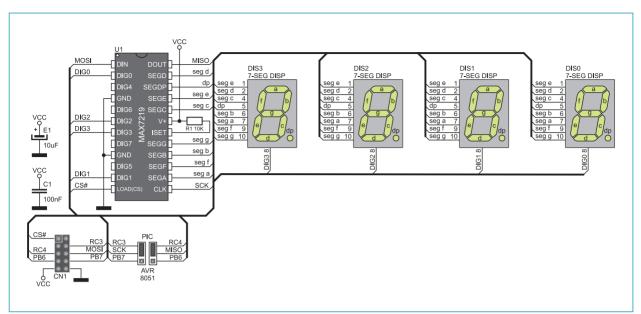


Figure 6: Serial 7-Seg Display additional board connection schematic

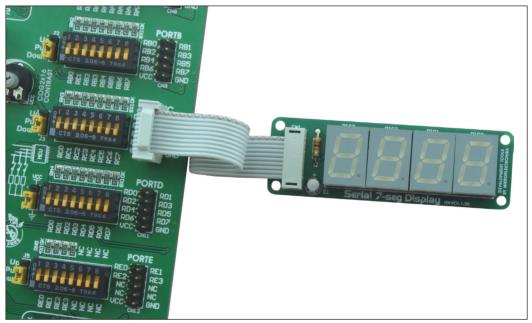


Figure 7: Serial 7-Seg Display additional board connected to a development system

If you want to learn more about our products, please visit our website at www.mikroe.com

If you are experiencing some problems with any of our products or just need additional information, please place your ticket at www.mikroe.com/en/support

If you have any questions, comments or business proposals, do not hesitate to contact us at office@mikroe.com

X-ON Electronics

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Daughter Cards & OEM Boards category:

Click to view products by MikroElektronika manufacturer:

Other Similar products are found below:

ADZS-21262-1-EZEXT 27911 SPC56ELADPT144S TMDXRM46CNCD DM160216 EV-ADUCM350GPIOTHZ EV-ADUCM350-BIO3Z

ATSTK521 1130 MA160015 MA180033 MA240013 MA240026 MA320014 MA330014 MA330017 TLK10034SMAEVM MIKROE
2152 MIKROE-2154 MIKROE-2381 TSSOP20EV DEV-11723 MIKROE-1108 MIKROE-1516 SPS-READER-GEVK AC244049

AC244050 AC320004-3 2077 ATSMARTCARD-XPRO EIC - Q600 -230 ATZB-212B-XPRO SPC560PADPT100S SPC560BADPT64S

MA180018 EIC - Q600 -220 AC164134-1 BOB-12035 STM8/128-D/RAIS AC164127-6 AC164127-4 AC164134-3 AC164156 MA320021

MA320024 DFR0285 DFR0312 DFR0356 MA320023 MIKROE-2564