

AEK-AUD-D903V1

Data brief

Class D automotive audio amplifier board with advanced diagnostics



Features

- With FDA903D class D automotive grade audio amp
- Mono channel up to 45 W
- Supports audio stream via I²S interface
- Configurable through dedicated I²C bus
- Dedicated DC diagnostic interrupt pin to signal faults
- Dedicated hardware MUTE pin
- Open load in play detection
- Short to Vcc / GND diagnostic
- Thermal protection
- Part of the AutoDevKit initiative
- RoHS compliant

Description

This evaluation board for the FDA903D 1 x 45 W class D digital input automotive power amplifier, with load current monitoring and wide voltage operation range, is highly suitable for typical automotive audio, infotainment and telematic applications in conjunction with suitable automotive microcontrollers.

The amplifier can also be interfaced with the SPC582B Chorus automotive microcontroller and can also provide Electric Vehicle Warning Sounds (or Acoustic Vehicle Alerting Systems, AVAS) solutions.

The FDA903D amplifier comes in a PowerSSO-36 slug-down package and features a configurable power limiting function, high-speed I²C and legacy mode interfaces, and an internal finite state machine.

The initial state of the device is the standby state from which it will not be possible to exit until the I2C interface has been correctly enabled: this means providing correct supply voltage, the I2S clock, the I2S data and a valid combination of enable pins in order to determine the I2C device address.

This system is required by new vehicles to alert pedestrians of the presence of electric powered vehicles that are generating much less noise. Warning sounds may be driver triggered (like a horn) or automatic mimicking engine sounds. From 2021 according to government regulations, the vehicle must make a continuous noise level of at least 56 dBA (within 2 meters) if the car is going 20 km/h (12 mph) or slower, and a maximum of 75 dBA.


Each combination of the Enable pins represents an address. Up to eight devices can be used in the same application with a single I2C bus. The internal I2C registers are pre-set in "default condition", waiting for the I2C next instruction. The return in Standby condition, (i.e. all enable pins at 0), will result in a reset for the amplifier. As defined in the finite state machine, the same event will happen if PLL is not locked, I2S is missing or not correct, Vcc is removed for system reset. FDA903D works only in I2C slave mode.

The combination of AEK-AUD-D903V1 with AEK-MCU-C1MLIT1 hosting SPC582B Chorus automotive microcontroller offers a viable low-cost solution for entry-level AVAS systems.

Product summary		
MCU discovery board for SPC5 Chorus 1M automotive microcontroller	AEK-MCU- C1MLIT1	
AutoDevKit library plugin for SPC5-STUDIO STSW- AutoDevKit		
1 x 45 W class D digital input automotive power amplifier with load current monitoring, wide voltage operation range for car audio and telematic - slug down version	FDA903D	


1 Block diagrams and schematic diagrams

1.1 Block diagrams

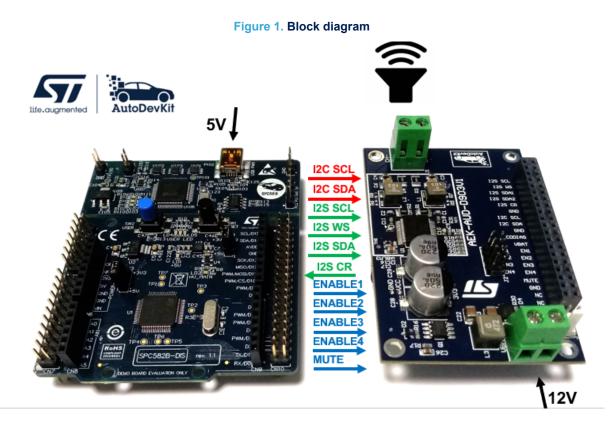

1.2 Schematic diagram

Figure 2. Schematic diagram

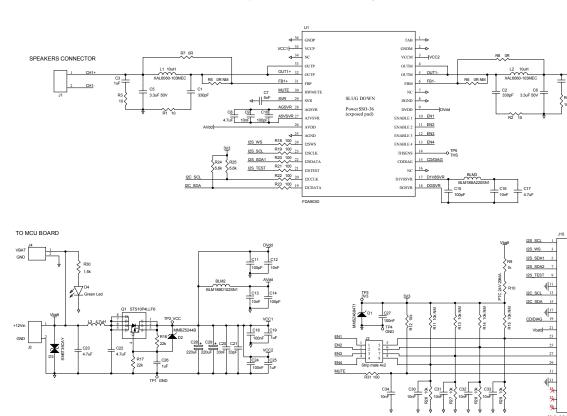

20x2 p2.54 STD DONGLE

Revision history

Table 1. Document revision history

Date	Version	Changes
24-Jun-2020	1	Initial release.

IMPORTANT NOTICE - PLEASE READ CAREFULLY

STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST's terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers' products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. For additional information about ST trademarks, please refer to www.st.com/trademarks. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2020 STMicroelectronics – All rights reserved

X-ON Electronics

Largest Supplier of Electrical and Electronic Components

Click to view similar products for Audio IC Development Tools category:

Click to view products by STMicroelectronics manufacturer:

Other Similar products are found below :

LM4906MMBD LM4935RLEVAL LME49710NABD LME49740MABD LME49740NABD LME49860MABD LME49870MABD EVAL-AD1940AZ EVAL-ADAU1401AEBZ SRC4382EVM-PDK TLV320AIC36EVM-K TPA5052EVM TPA6136A2YFFEVM LM4562HABD LM4906LDBD LM4923LQBD LM4992SDBD LME49710MABD LME49713MABD LME49860NABD MAX98300EVKIT+WLP MAX9738EVKIT+ MAX98358EVSYS#WLP MAX9723DEVKIT+ EVAL-ADAV803EBZ LM4809MBD LM4674TLBD CDBWM8725-M-1 CDBWM8533-M-1 EV_ICS-40740-FX SDCK3 PIM524 MAX9723DEVCMODU+ DEV-17737 MAX9850EVCMOD2# EVALAHNBIM69D130V01TOBO1 1063 TAS5756MDCAEVM TLV320ADC3101EVM-K TLV320AIC3007EVM-K TLV320AIC3105EVM-K TLV320AIC3253EVM-K TPA2016D2EVM TPA2035D1EVM TPA2051D3YFFEVM TPA3107D2EVM TPA6120A2EVM TPA6132A2EVM2 MIKROE-2454 1381